



Passive Circuits





Passive Circuits

- Batteries

- Voltages range from $\sim 1.3\text{V}$ to 180V

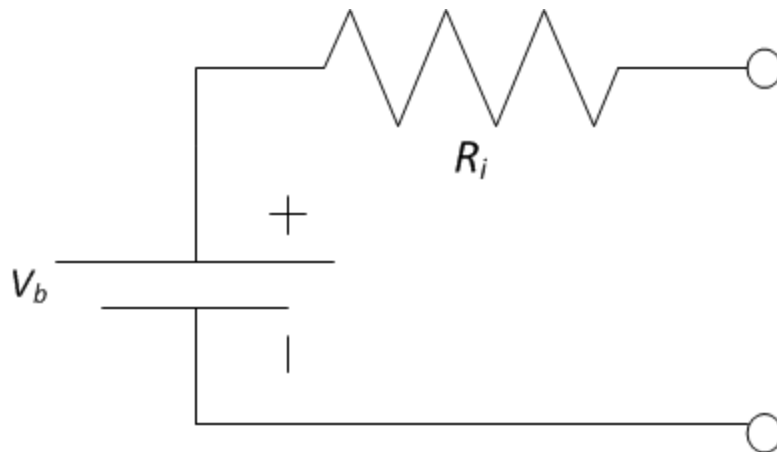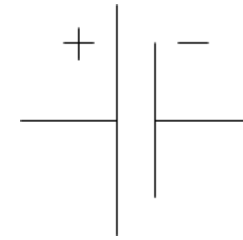- Internal resistance $I_{max} = \frac{V_b}{R_i}$



Voltage at terminals

$$V_{out} = V_b - IR_i$$



An ideal battery has zero internal resistance.



Passive Circuits

- Kirchhoff's Current Law

Charge is not allowed to pile up at nodes, or

The total current entering any node is equal to the total current leaving that node.

$$\sum_{nodes} I_{node} = 0$$



Passive Circuits

- Kirchhoff's Voltage Law

The sum of all of the source voltages in a closed path (loop) is equal to the sum of the voltage drops in that loop.


$$\sum_{loop} V_{loop} = 0$$




Passive Circuits

- Resistor Networks

Voltage Divider


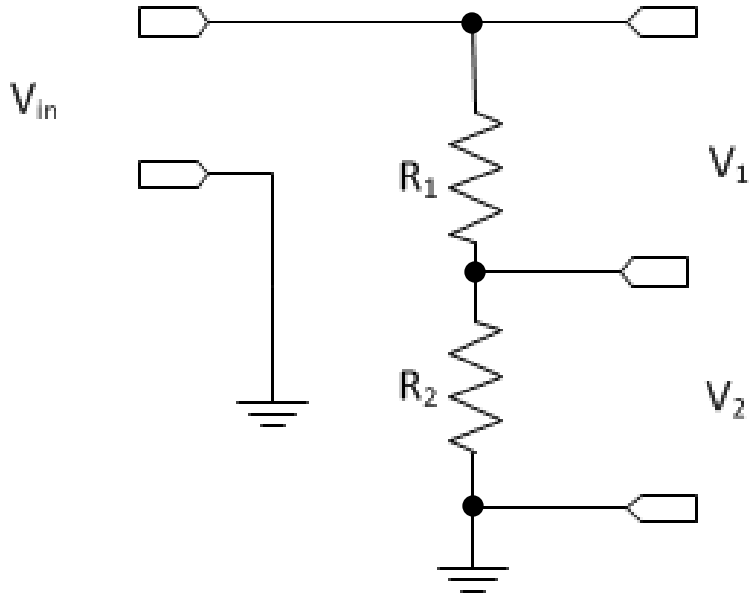


Same As

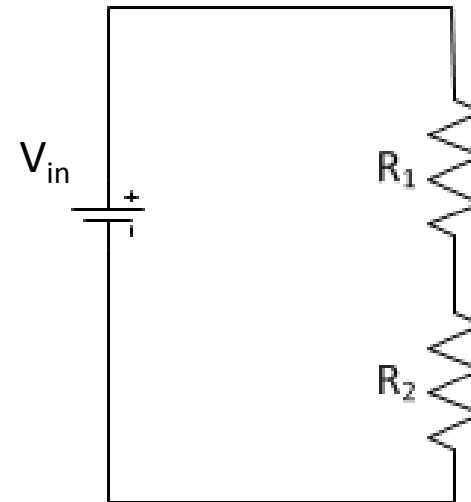



Passive Circuits

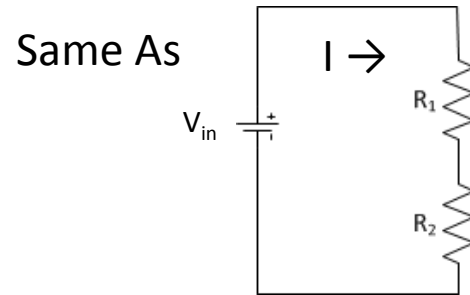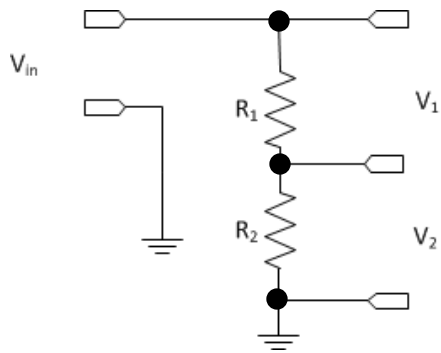

$$R_{\text{total}} = R_1 + R_2$$

$$V_1 = I R_1$$

$$V_2 = I R_2$$

$$V_{\text{in}} = V_1 + V_2 = I R_{\text{total}} = I (R_1 + R_2)$$

$$\text{So } I = \frac{V_{\text{in}}}{R_1 + R_2}$$


$$\text{And } V_1 = V_{\text{in}} \frac{R_1}{R_1 + R_2} \text{ \& } V_2 = V_{\text{in}} \frac{R_2}{R_1 + R_2}$$



Passive Circuits

- Resistor Networks

Voltage Divider

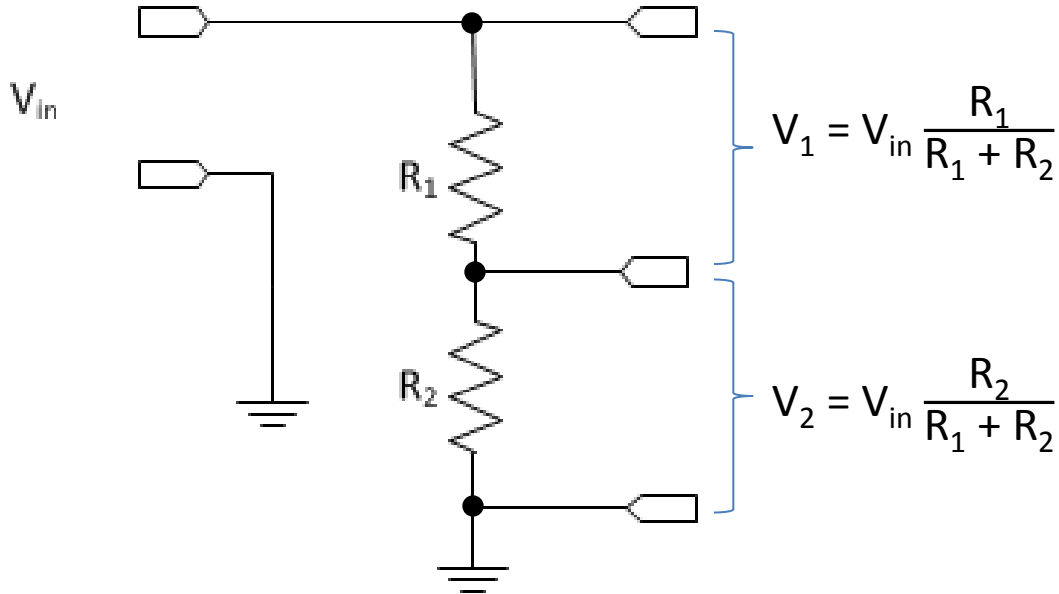




Passive Circuits

- Resistor Networks

Voltage Divider

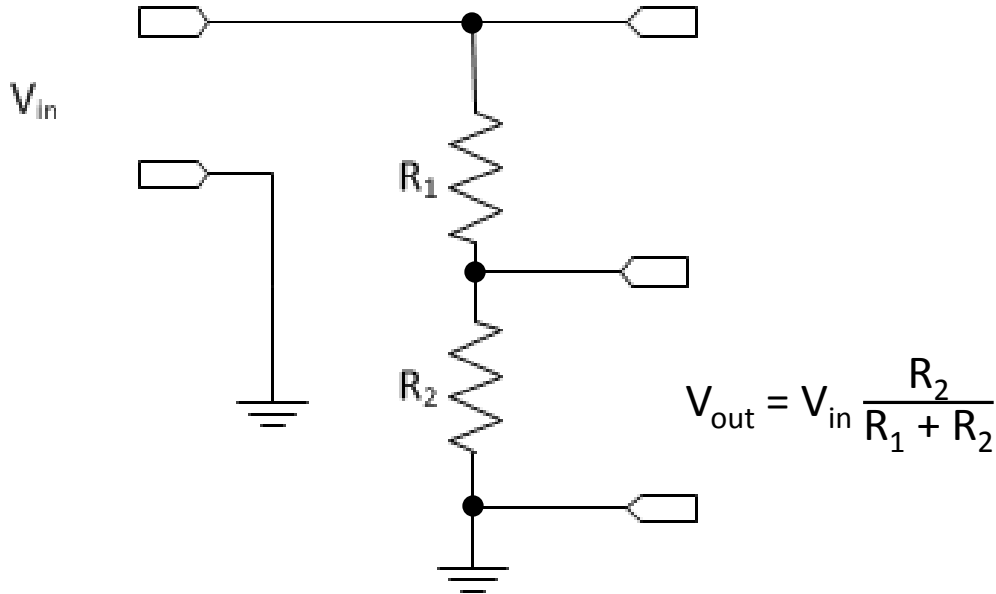


Note: There's an infinite number of valid solutions for R_1 & R_2 .



Passive Circuits

- Resistor Networks

Voltage Divider

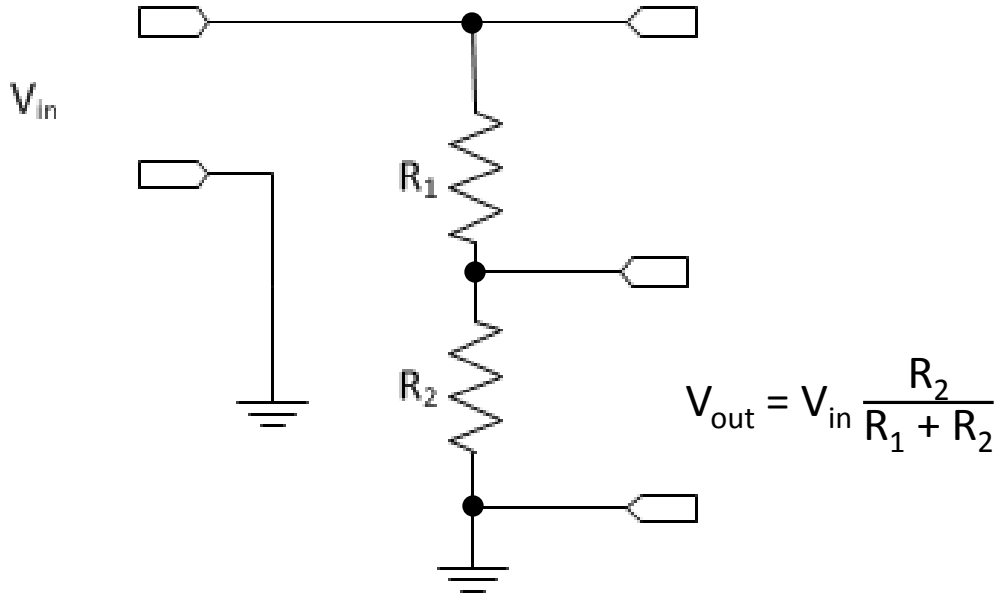

Suppose $V_{in} = 10$ volts, and I want an output voltage of 2 volts.

Even with the constraint that $\frac{R_2}{R_1 + R_2} = \frac{1}{5}$, there's an infinite number of valid possible values of R_1 & R_2 .

Whadda ya do?


This is dilemma is very common in electronics.



Passive Circuits

- Resistor Networks

Voltage Divider

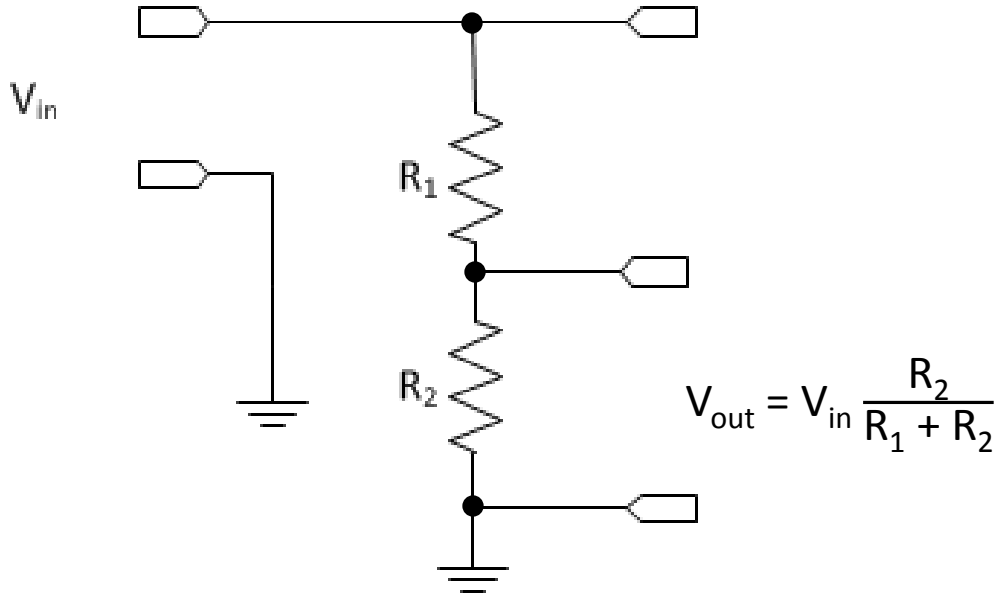

Make an arbitrary decision.

Secondary considerations – we might want to be energy efficient. Power loss in the divider is

$$P_{\text{loss}} = \frac{V_{\text{in}}^2}{R_1 + R_2}$$


So you can increase energy efficiency by increasing $(R_1 + R_2)$.



Passive Circuits

- Resistor Networks

Voltage Divider

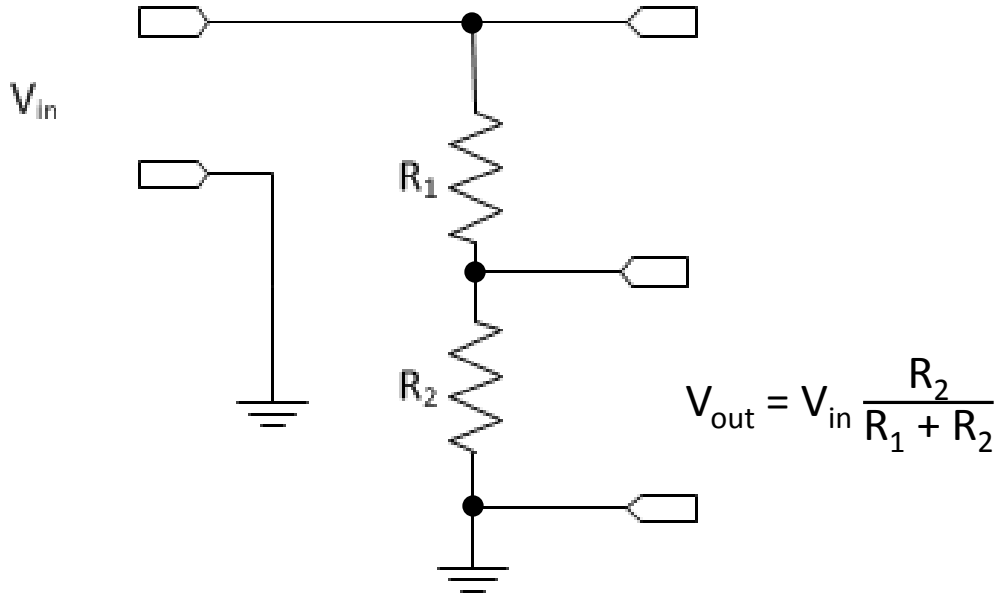

Make an arbitrary decision.

Secondary considerations –

So you can increase energy efficiency by increasing $(R_1 + R_2)$.


BUT... You need R_1 & R_2 to be low enough that whatever circuit you attach to V_{out} does not itself draw enough current to void our voltage divider equation. (i.e. “short” R_2)



Passive Circuits

- Resistor Networks

Voltage Divider

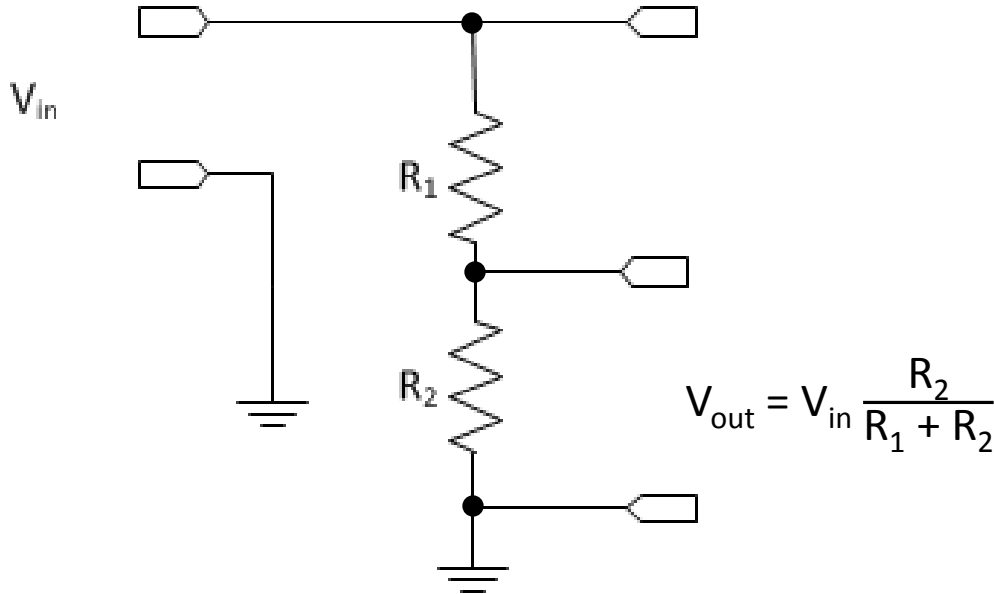

Make an arbitrary decision.

Secondary considerations –
Thermal noise from a
resistance (R):

$$V_{\text{RMS}} = \sqrt{4k_B T R \Delta f}$$


Δf = frequency range



Passive Circuits

- Resistor Networks

Voltage Divider

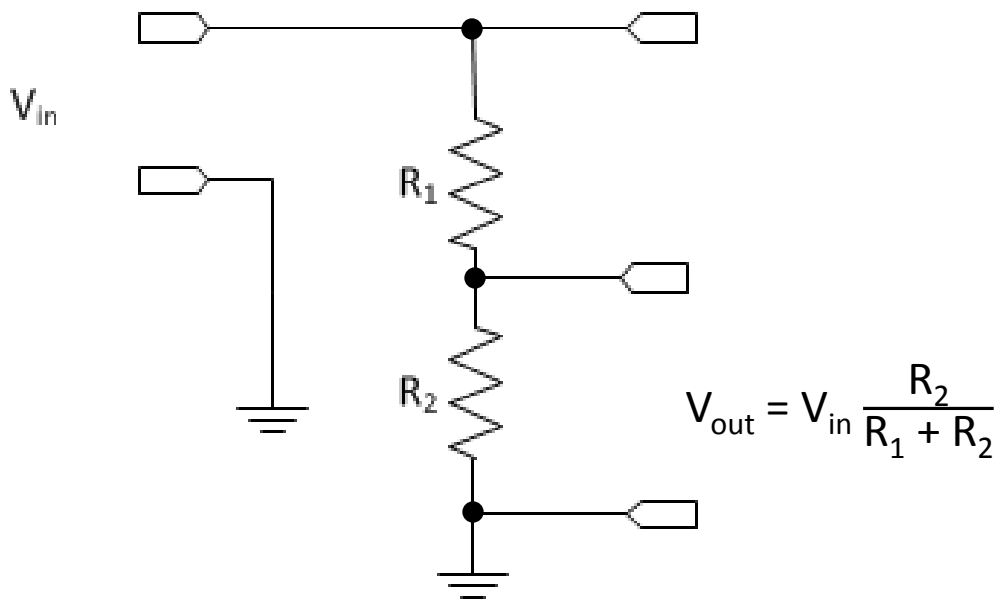

Make an arbitrary decision.

So generally one has to pick a value of $(R_1 + R_2)$ that isn't too large and isn't too small. That choice depends on what you will do with V_{out} .



Passive Circuits

- Impedance

$$Z = R + i\chi \quad \text{where } i = \sqrt{-1}, \chi \text{ is called the reactance}$$

Engineers use j instead of i .
H & H uses j .

For a resistor, $Z = R$

For a capacitor of capacitance C , $\chi = \frac{i}{\omega C}$

For an inductor of inductance L , $\chi = -i\omega L$


$$\text{Generalized Ohm's Law: } Z(\omega) = \frac{V(\omega)}{I(\omega)}$$



Passive Circuits

Thevenin's Theorem

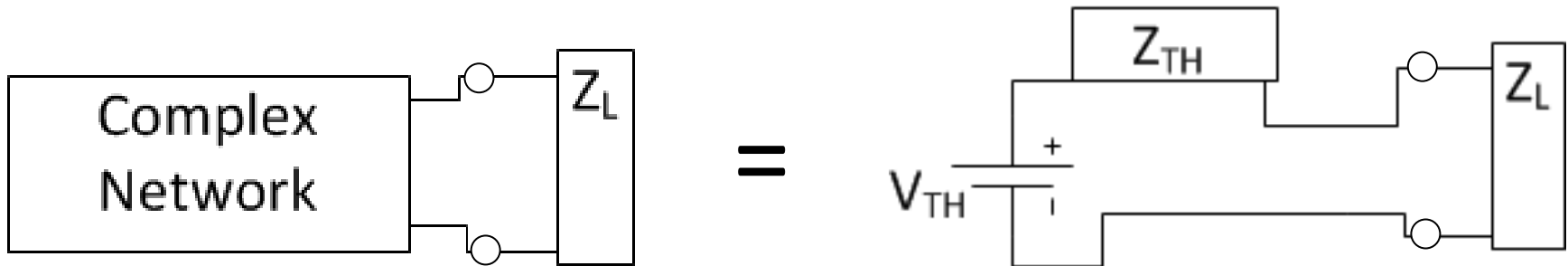
We can convert any impedance Z_L , connected to two terminals of a network into an equivalent voltage source (V_{TH}) in series with an impedance Z_{TH} , connected to that Z_L .





Passive Circuits

Thevenin's Theorem

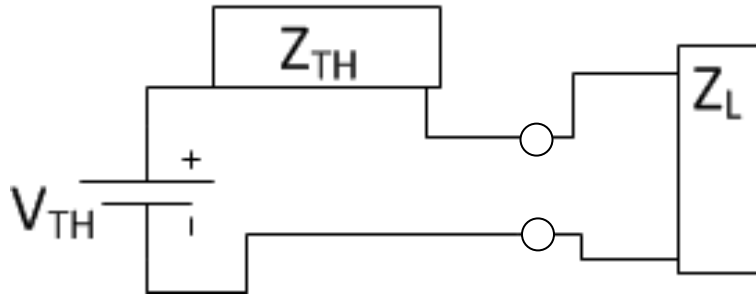



V_{TH} = open circuit voltage of terminals with Z_L not connected.

Z_{TH} = impedance looking into terminals
= "output impedance"



Passive Circuits

Thevenin's Theorem

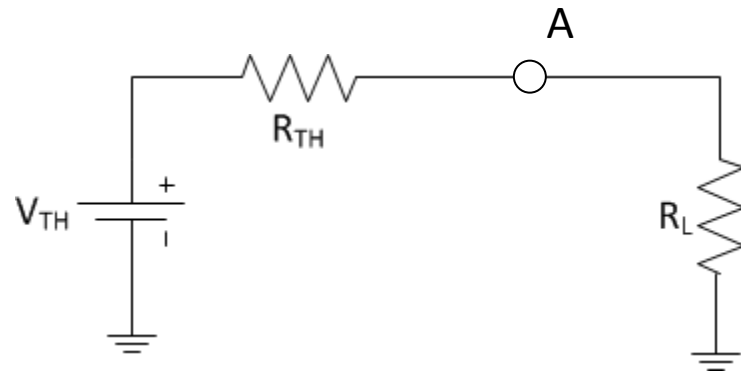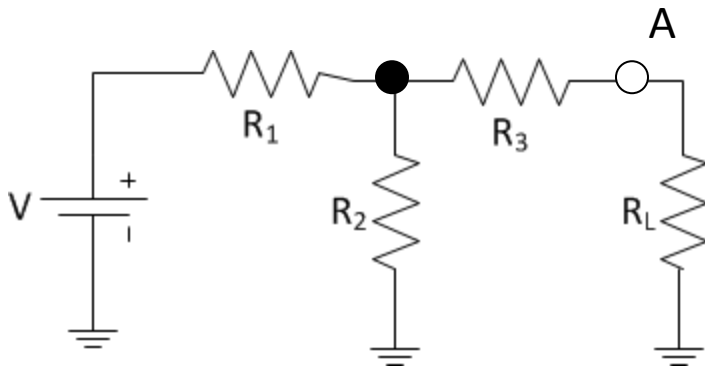

$$V_{TH} = V_A \text{ without } R_L$$

Without R_L , circuit is just a voltage divider formed by R_1 & R_2 .

$$\text{So } V_{TH} = V \frac{R_2}{R_1 + R_2}$$




Passive Circuits

Thevenin's Theorem

What about R_{TH} ?

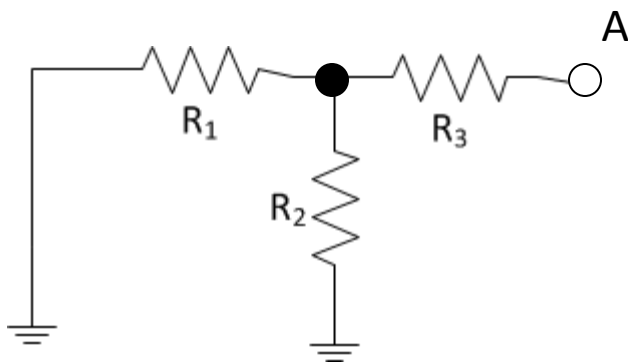Remember, ideal batteries (ideal voltage sources) have zero internal resistance. So, “looking at terminal A with R_L not connected” looks like:



So

$$R_{TH} = R_3 + \underbrace{R_1 || R_2}$$



Shorthand for “ R_1 in parallel with R_2 ”.

$$\frac{1}{R_1 || R_2} = \frac{1}{R_1} + \frac{1}{R_2}$$



Passive Circuits

Thevenin's Theorem

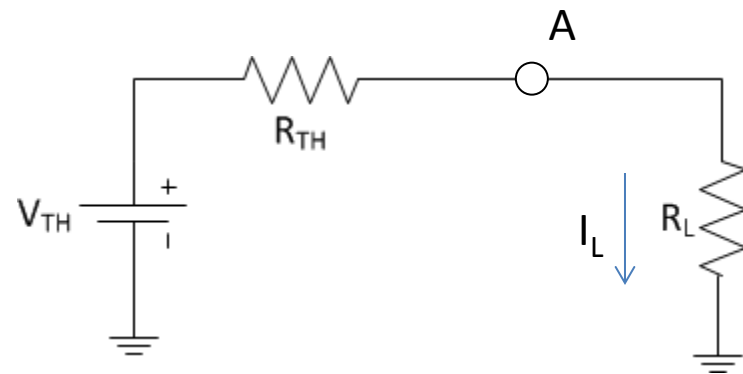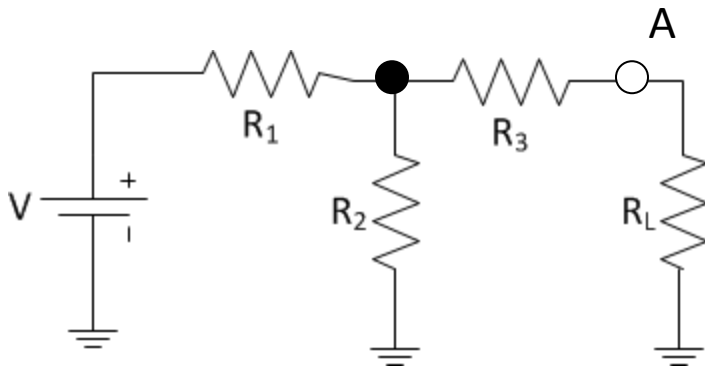

Short the output ($R_L = 0$)


$$I_L = \frac{V_{TH}}{R_L + R_{TH}}$$



Passive Circuits

Norton's Theorem

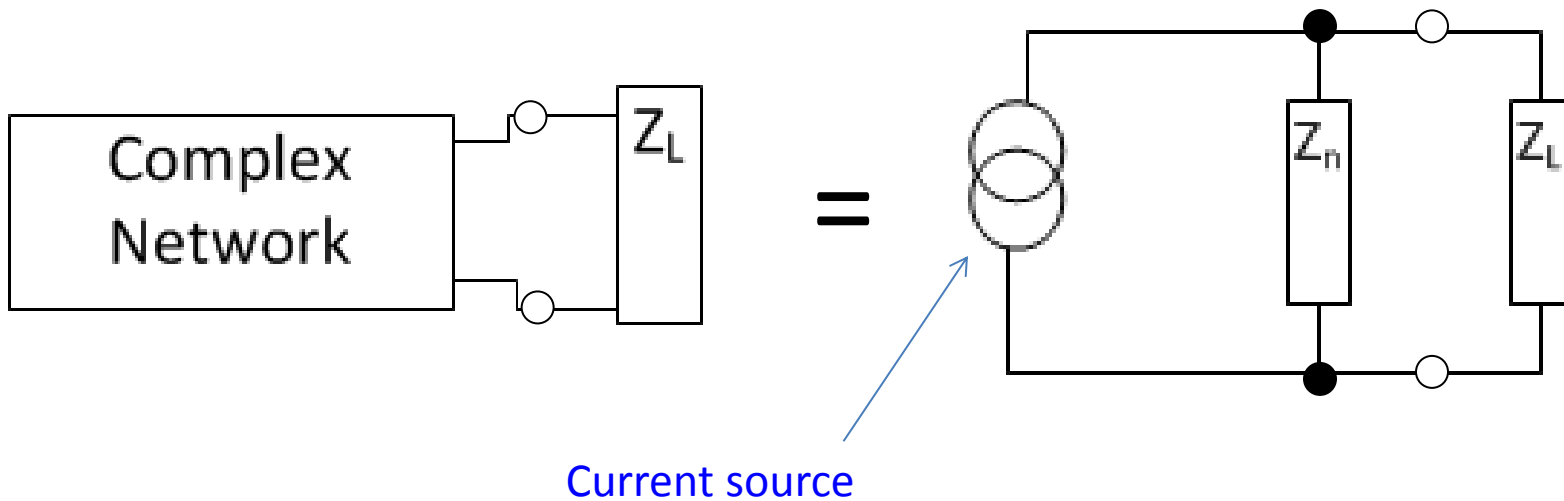
The current through any impedance Z_L , connected to two terminals of a network is the same as if Z_L were connected in parallel with another impedance Z_n and a current source I_n .





Passive Circuits

Norton's Theorem

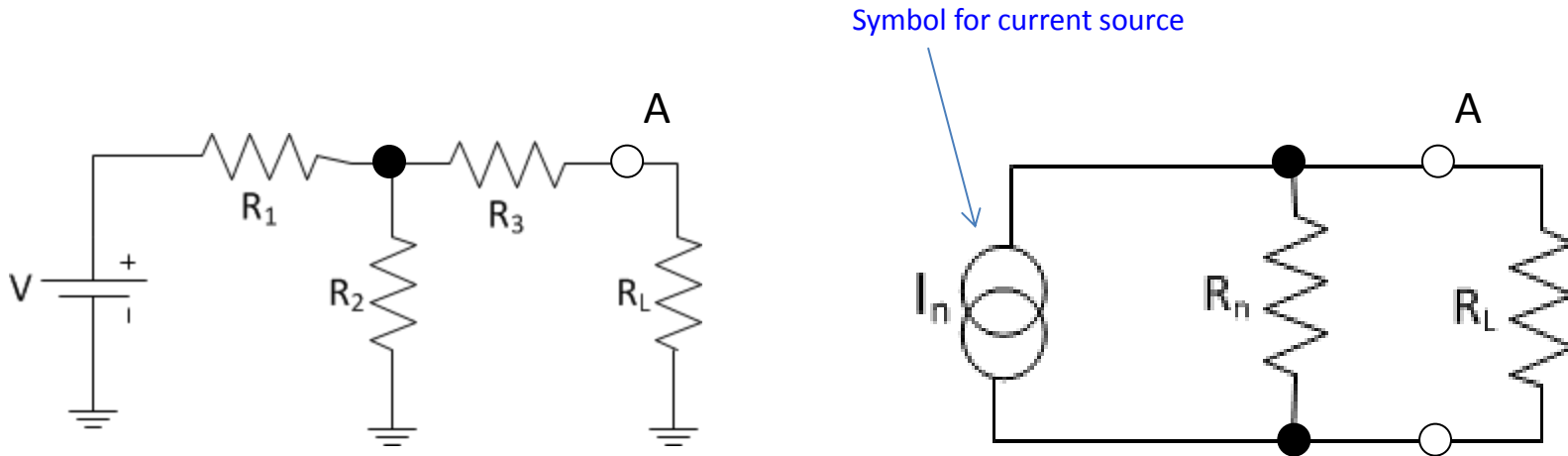

Current through R_L is I_L . Current splits each path in proportion of its resistance to the total resistance.

$$I_L = I_n \frac{R_n}{R_n + R_L} \quad (\text{current divider})$$

Open circuit (R_L gone) requires $V = I_n R_n$



Passive Circuits

We know $V_{TH} = V = I_n R_n$

In both pictures of this circuit, we know $I_L = I_L$

Thevenin

$$I_L = \frac{V_{TH}}{R_L + R_{TH}}$$

=

Norton

$$I_n \frac{R_n}{R_n + R_L}$$

Plug in $V_{TH} = V = I_n R_n$

$$I_L = \frac{I_n R_n}{R_L + R_{TH}}$$

=

$$I_n \frac{R_n}{R_n + R_L}$$

Results in

$$R_L + R_{TH} = R_n + R_L$$

$$R_{TH} = R_n$$

Since both R_{TH} & R_n represent the resistance “looking at” the circuit at the same point, they better be the same.



AC Circuits & Circuits

Standard physics notation

Steady “Sine” Wave Oscillation:

$$V = A e^{-i\omega t} = A (\cos \omega t - i \sin \omega t)$$

Standard stuff: $\omega = 2\pi f$ f = frequency [f] = Hz $[\omega] = \text{rad/sec}$

We always only observe the real part



AC Circuits & Circuits

Resistors:

$$V = IR$$


$$I = \frac{A}{R} e^{-i\omega t} \rightarrow (\text{real}) \quad \frac{A}{R} \cos \omega t \quad I \text{ \& V are in phase}$$

Capacitors:

$$V = \frac{Q}{C} \quad I = \frac{dQ}{dt} = C \frac{dV}{dt}$$

$$\text{So } I = -i\omega CA e^{-i\omega t} = -i\omega CA (\cos \omega t - i \sin \omega t)$$

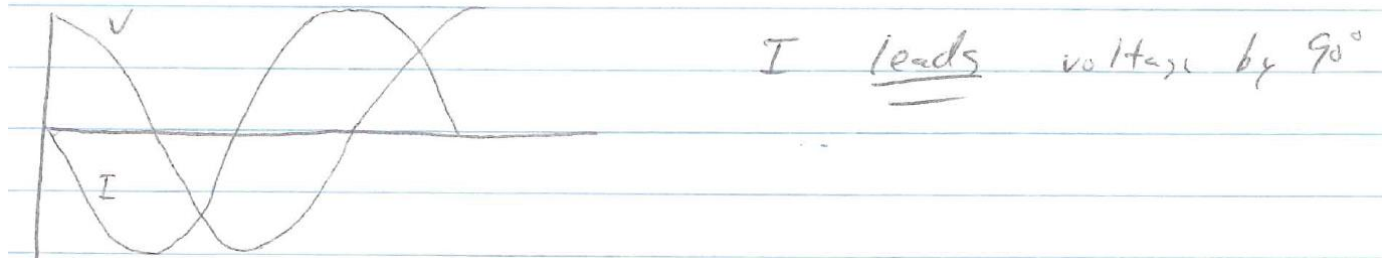Real part of I : $-\omega CA \sin \omega t$





AC Circuits & Circuits

Capacitors (*cont*):

Define the capacitance reactance (χ_c) so we can write an “ohms law”:

$$V = I \chi_c$$

We just saw that $I = -i\omega CA e^{-i\omega t}$ for a voltage $A e^{-i\omega t}$,

So $I = -i\omega CV$ which means

$$V = -i\omega CV \chi_c$$

So

$$\chi_c = \frac{1}{-i\omega C} = \frac{-1}{i\omega C}$$

The impedance of a capacitor decreases with increasing capacitance & increasing frequency.

As frequency goes up, capacitors start to look like short circuits.




AC Circuits & Circuits

Inductors:

$$V = L \frac{dI}{dt} \quad \text{which means } I = \frac{1}{L} \int V dt$$

$$\text{So } I = \frac{A}{-i\omega L} e^{-i\omega t}$$
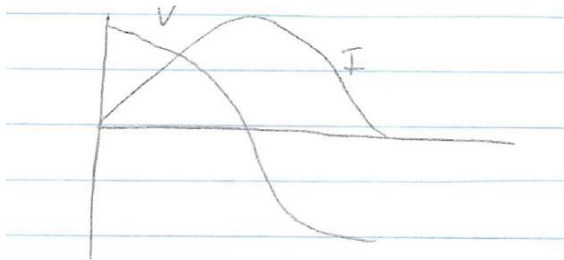
$$\text{Real part of } I: = \frac{A}{\omega L} \sin \omega t$$



Current lags voltage by 90°

$$V = I \chi_c$$

$$V = \frac{V}{-i\omega L} \chi_c$$

$$\text{So } \chi_c = -i\omega L$$

The impedance of a inductor increases with increasing inductance & increasing frequency.


As frequency goes up, inductors start to look like open circuits.



AC Circuits & Circuits

Impedance Plot:

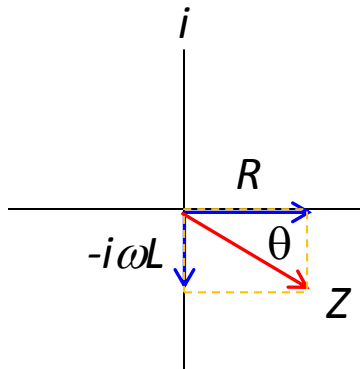Z of a R,L,C circuit is the vector sum of the amplitudes. Phase angle is the angle between current & voltage.



R + L in series

$$Z = R - i\omega L$$


$$|Z| = \sqrt{R^2 + \omega^2 L^2}$$

$$\theta = \tan^{-1} \frac{-\omega L}{R}$$



AC Circuits & Circuits

R + C in series

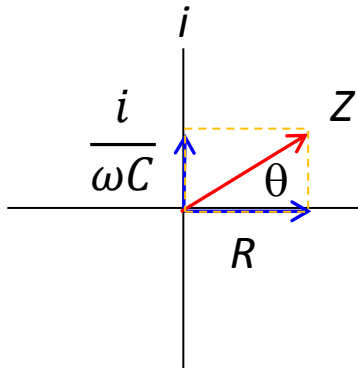

$$Z = R - \frac{i}{\omega C}$$


$$|Z| = \sqrt{R^2 + \frac{1}{\omega^2 C^2}}$$

$$\theta = \tan^{-1} \frac{1}{R\omega C}$$



AC Circuits & Circuits

Resonance Circuits R, C, L series

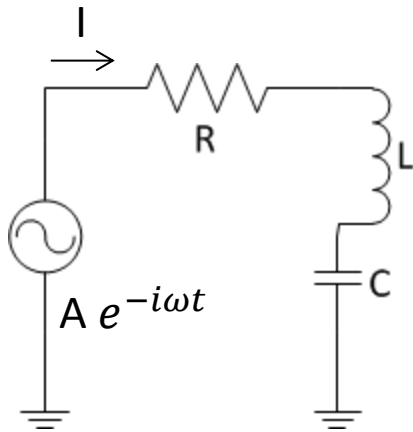

$$0 = V_{\text{total}} - V_R - V_C - V_L$$


$$0 = A e^{-i\omega t} - IR - L \frac{dI}{dt} - \frac{Q}{C}$$

$$A e^{-i\omega t} = IR + L \frac{dI}{dt} + \frac{Q}{C}$$

We could solve this the usual (algebraic) way, but there's another way.

$$Z = Z_R + Z_L + Z_C \rightarrow Z = R - i\omega L + \frac{i}{\omega C}$$



$$|Z| = \sqrt{R^2 + \left(\frac{1}{\omega C} - \omega L\right)^2}$$

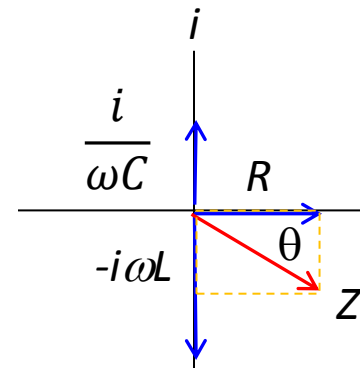



AC Circuits & Circuits

Resonance Circuits R, C, L series

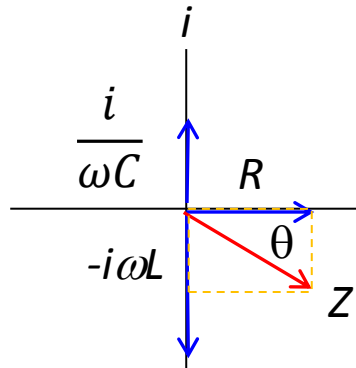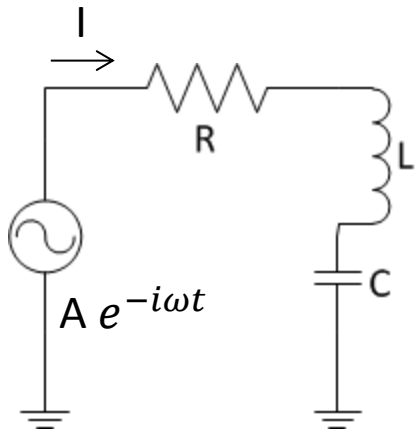

$$Z = R - i\omega L + \frac{i}{\omega C}$$

Ohm's Law $I = \frac{V}{Z}$

$$I = \frac{A e^{-i\omega t}}{Z}$$

The current is a maximum when $|Z|$ is a minimum.

Why? $||I|| = \left| \frac{A e^{-i\omega t}}{Z} \right| = \frac{A}{|Z|}$

For fixed L, R & C, this occurs if we can make


$$Z = R - i\omega L + \frac{i}{\omega C} = R \quad \text{or} \quad \omega L = \frac{1}{\omega C} \quad \text{or} \quad \omega = \omega_o \equiv \frac{1}{\sqrt{LC}}$$



AC Circuits & Circuits

Resonance Circuits R, C, L series

$$\omega_0 \equiv \frac{1}{\sqrt{LC}}$$

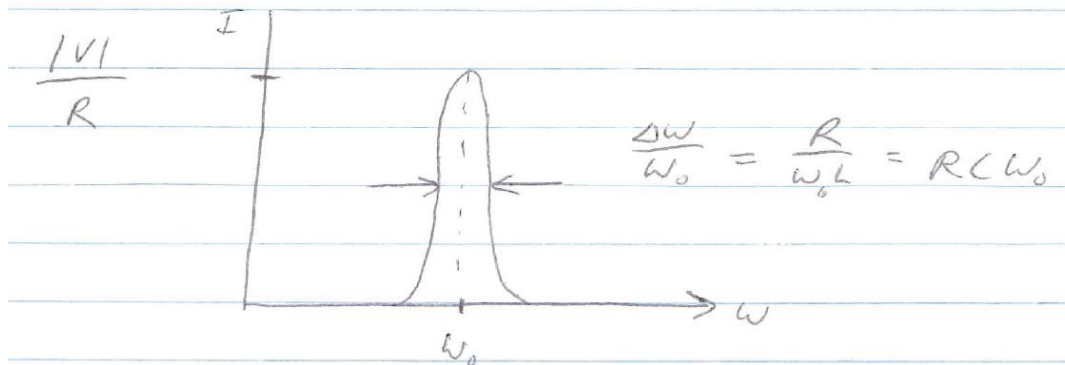


The “Q” or “quality factor” of any resonating thing = $\frac{\omega_0}{\Delta\omega}$

$$\text{For this case, } Q = \frac{\omega_0}{\Delta\omega} = \frac{\omega_0 L}{R} = \frac{1}{\omega_0 RC}$$



AC Circuits & Circuits

Resonance Circuits R, C, L parallel

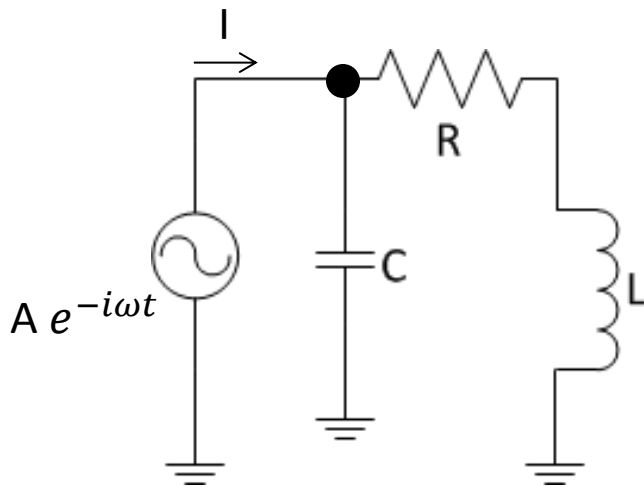

$$\frac{1}{Z_{||}} = \frac{1}{Z_C} + \frac{1}{Z_R + Z_L}$$

$$Z_R = R, Z_C = \chi_C = \frac{i}{\omega C} \text{ and } Z_L = \chi_L = -i\omega L$$

So


$$\frac{1}{Z_{||}} = -i\omega C + \frac{1}{R - i\omega L}$$

$$Z_{||} = \frac{R - i\omega L}{1 - i\omega CR - \omega^2 LC}$$



AC Circuits & Circuits

Resonance Circuits R, C, L parallel

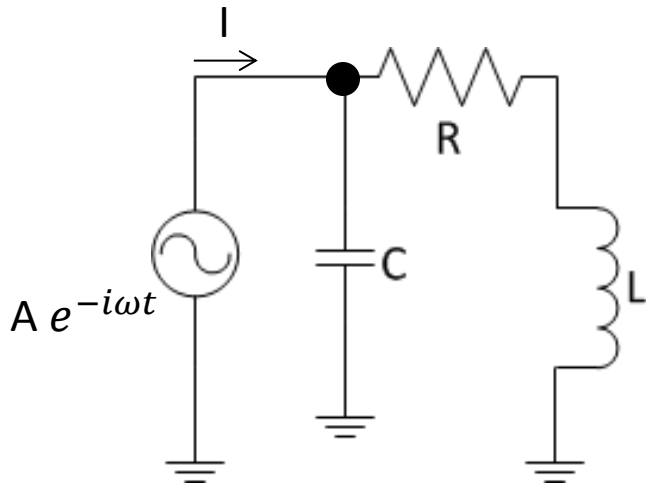

$$Z_{||} = \frac{R - i\omega L}{1 - i\omega C R - \omega^2 L C}$$

$$|Z_{||}| = \sqrt{\frac{R^2 + \omega^2 L^2}{\omega^2 R^2 C^2 + (1 - \omega^2 L C)^2}}$$

Again, $|Z_{||}|$ is a maximum when

$$\omega = \omega_o \equiv \frac{1}{\sqrt{LC}}$$


When $R \ll \omega L$:
$$\frac{1}{Z_{||}} = -i\omega C + \frac{1}{-i\omega L} = i(1 - \omega^2 LC)/\omega CL$$

$$|Z_{||}| \sim \sqrt{\frac{\omega^2 L^2}{(1 - \omega^2 LC)^2}} = \frac{\omega L}{1 - \omega^2 LC} \rightarrow \infty \text{ as } \omega \rightarrow \omega_o$$




AC Circuits & Circuits

Resonance Circuits R, C, L parallel

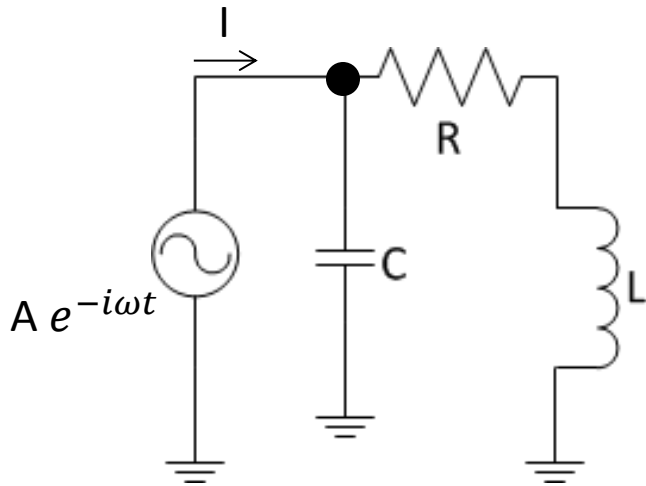

When $R \ll \omega L$:


$$|Z_{||}| \sim \sqrt{\frac{\omega^2 L^2}{(1 - \omega^2 LC)^2}} = \frac{\omega L}{1 - \omega^2 LC} \rightarrow \infty \text{ as } \omega \rightarrow \omega_0$$

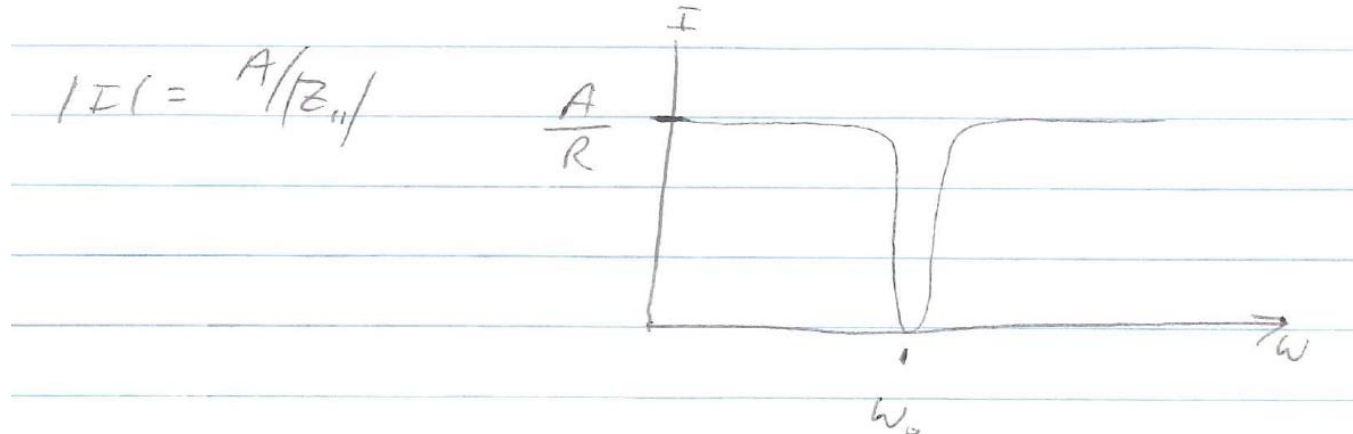



AC Circuits & Circuits

Filters

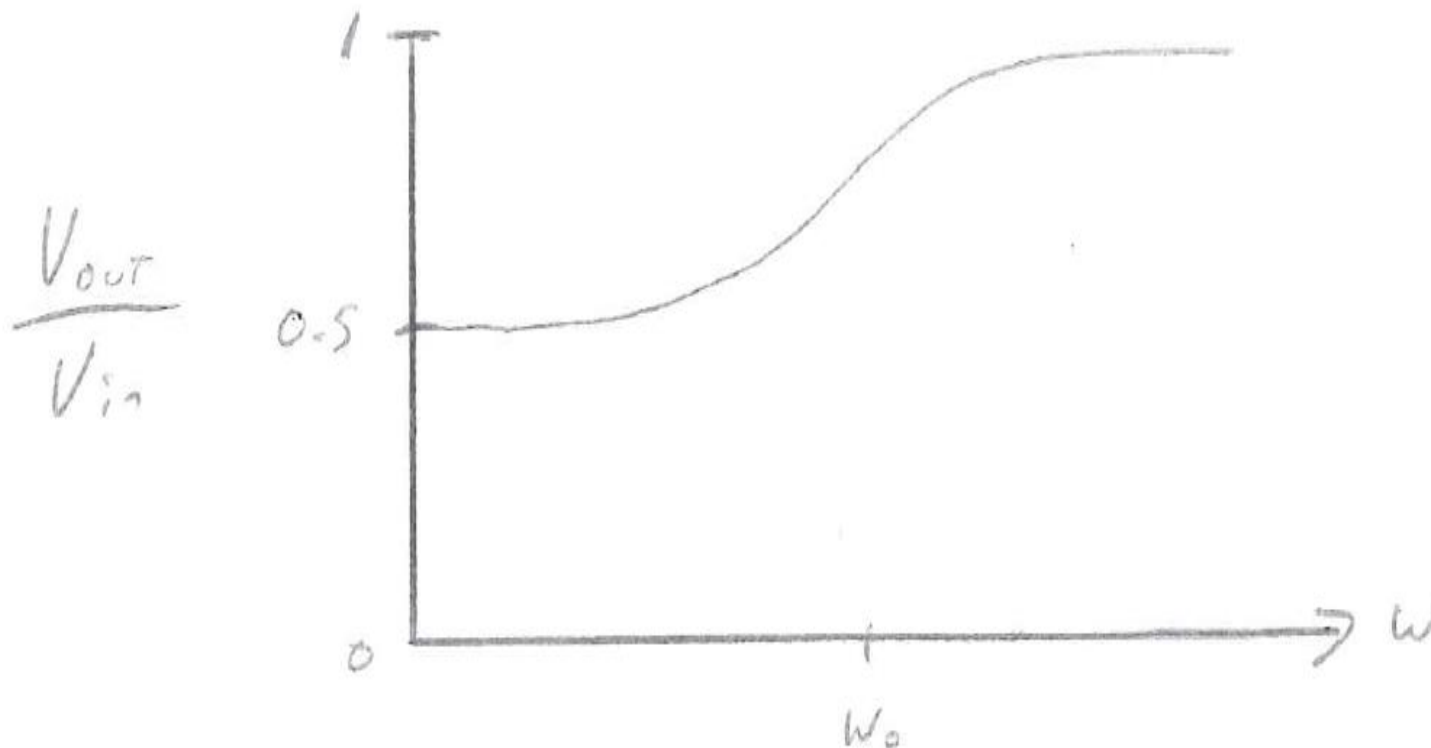


$\omega_0 = \frac{1}{\tau}$ where τ is some time constant (like an "RC" time constant) that you set.




AC Circuits & Circuits

Filters

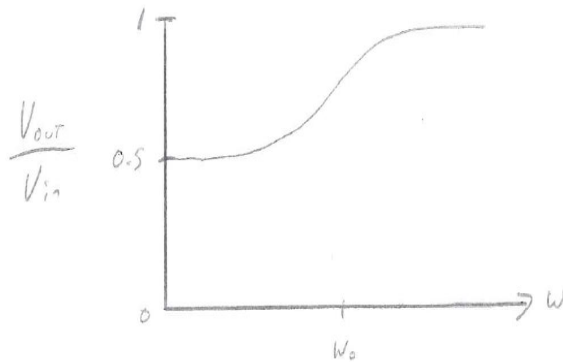

At $\omega = 0$, we know a filter with this behavior must just divide to voltage by $\frac{1}{2}$.

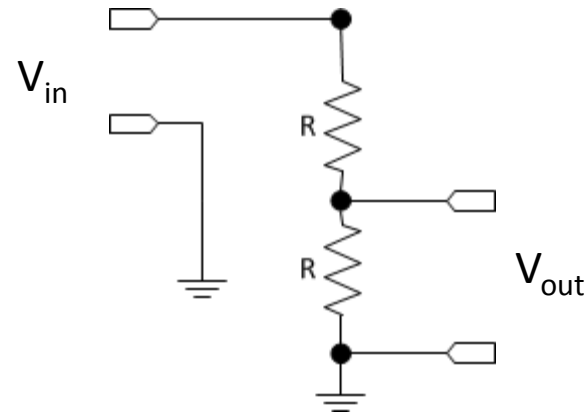
So at $\omega = 0$, we know it must look something like this:





AC Circuits & Circuits


Filters

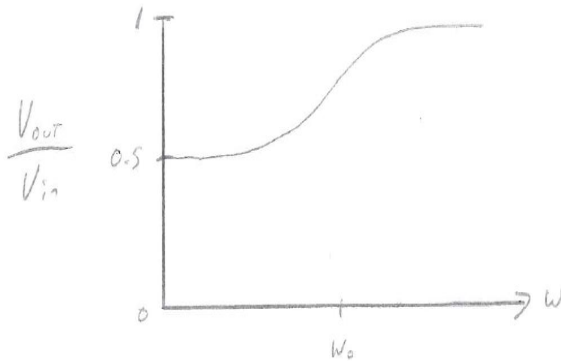

At $\omega = \infty$, we know the signal must bypass the top R so that the divider does not divide anymore.

We know the impedance of capacitors is ∞ at $\omega = 0$, & 0 at $\omega = \infty$.

So we can do something like this:

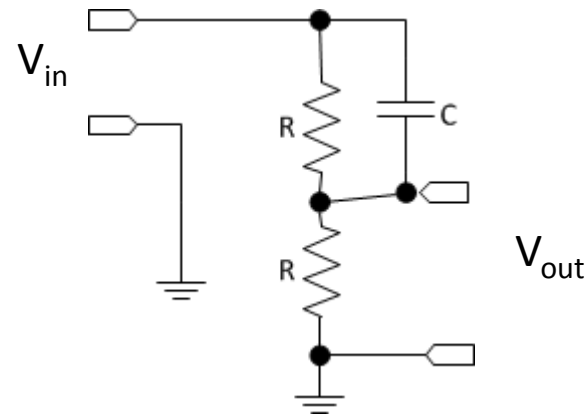




AC Circuits & Circuits


Filters

So what is ω_0 ? Use Thevenin's Theorem.

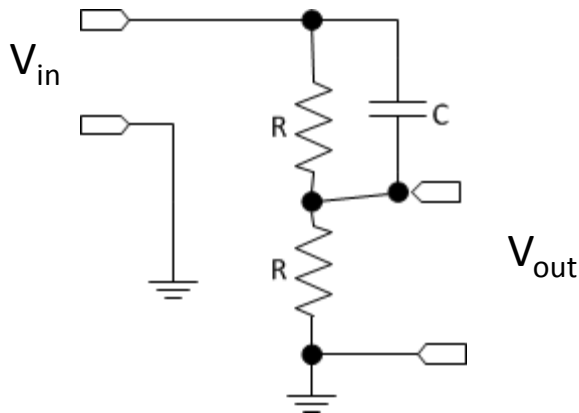Ideal voltage sources have zero impedance. (They put out up to infinite current to hold voltage steady – no internal resistance.)




Looks like:

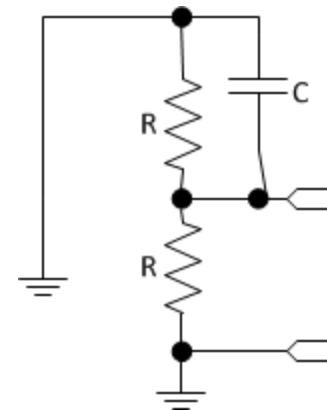



AC Circuits & Circuits

Filters

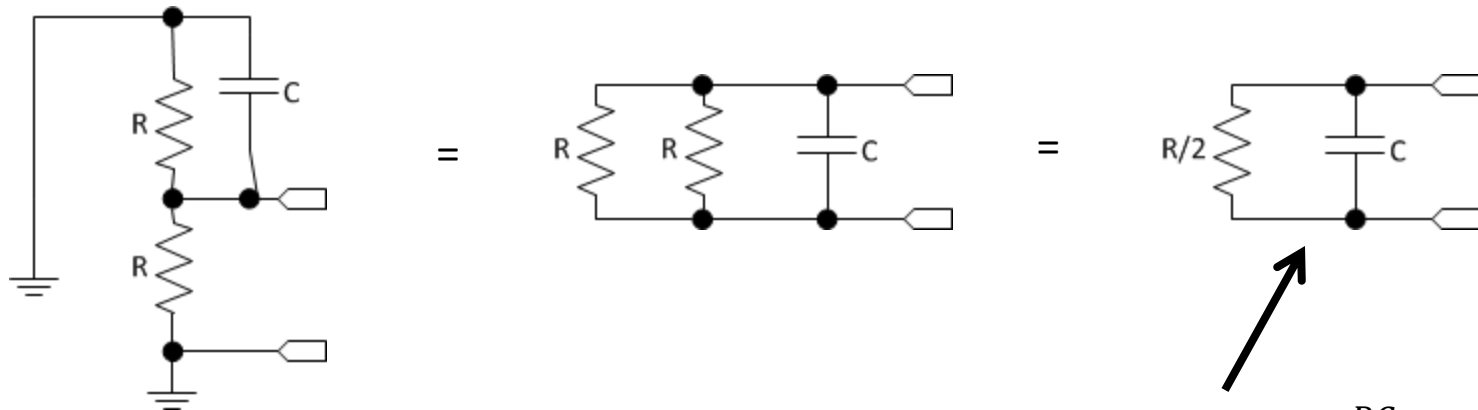



This you know has an RC time constant τ of $\frac{RC}{2}$

$$\omega_0 = \frac{1}{\tau} \text{ so } \omega_0 = \frac{2}{RC}$$




AC Circuits & Circuits

Filters

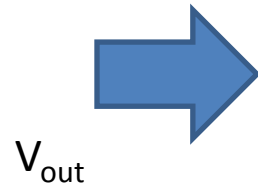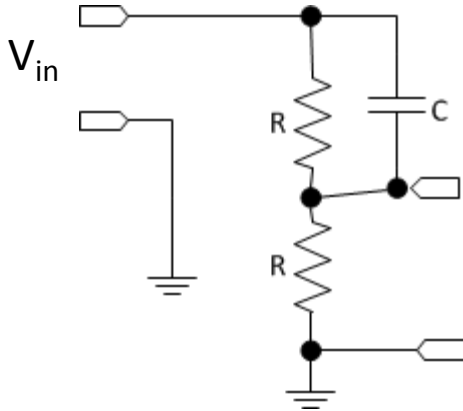

$$\frac{V_{out}}{V_{in}}$$

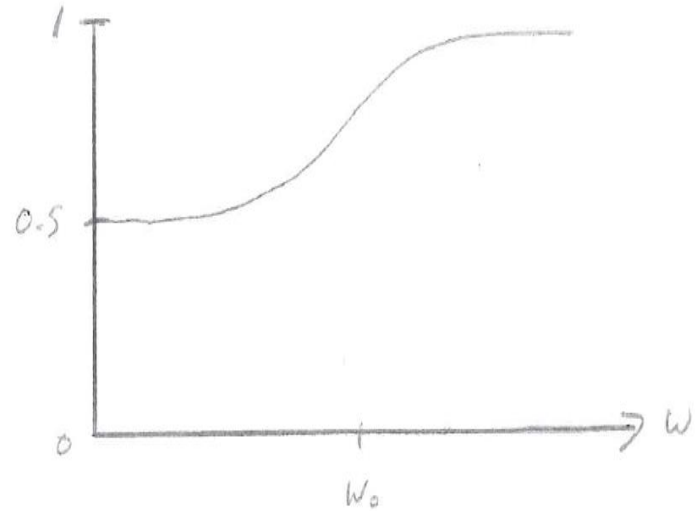

$$\omega_0 = \frac{1}{\tau} \text{ SO } \omega_0 = \frac{2}{RC}$$