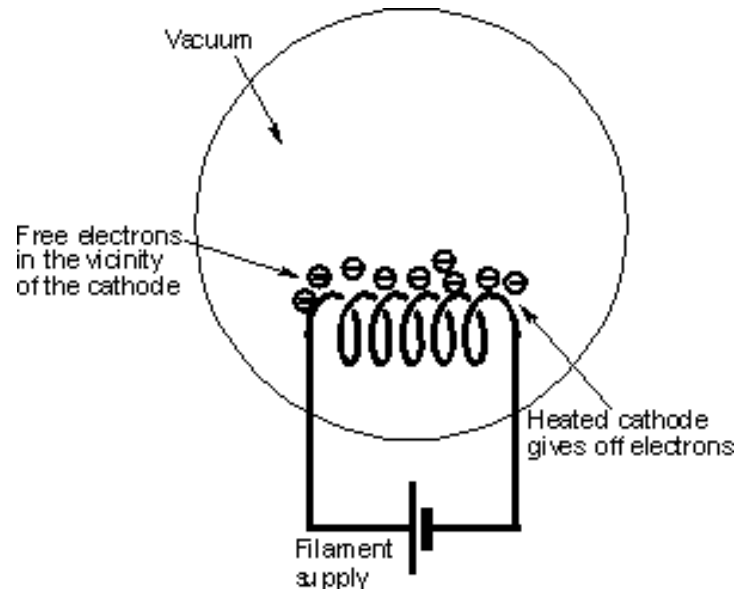




Semiconductors


Vacuum Tubes





Semiconductors


Vacuum Tubes

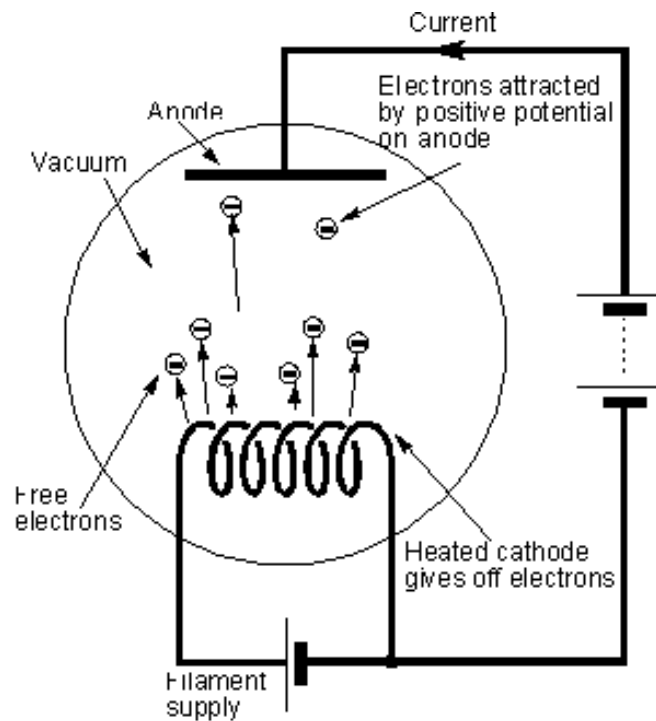



Semiconductors

Vacuum Tubes

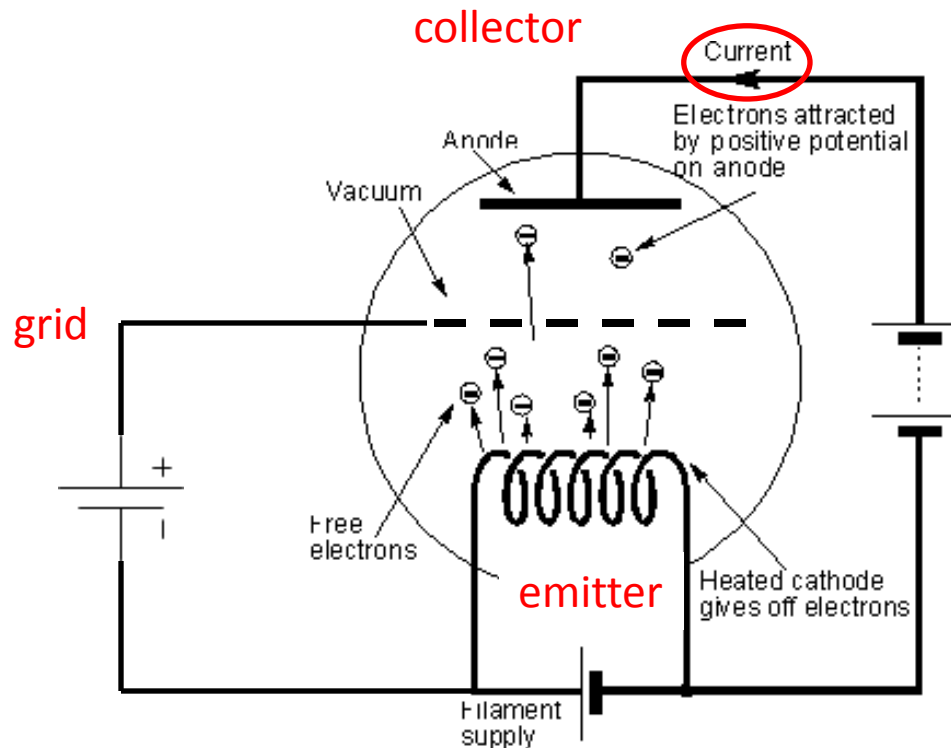


Small voltage on grid can block large current between emitter & collector.




Semiconductors

Vacuum Tubes

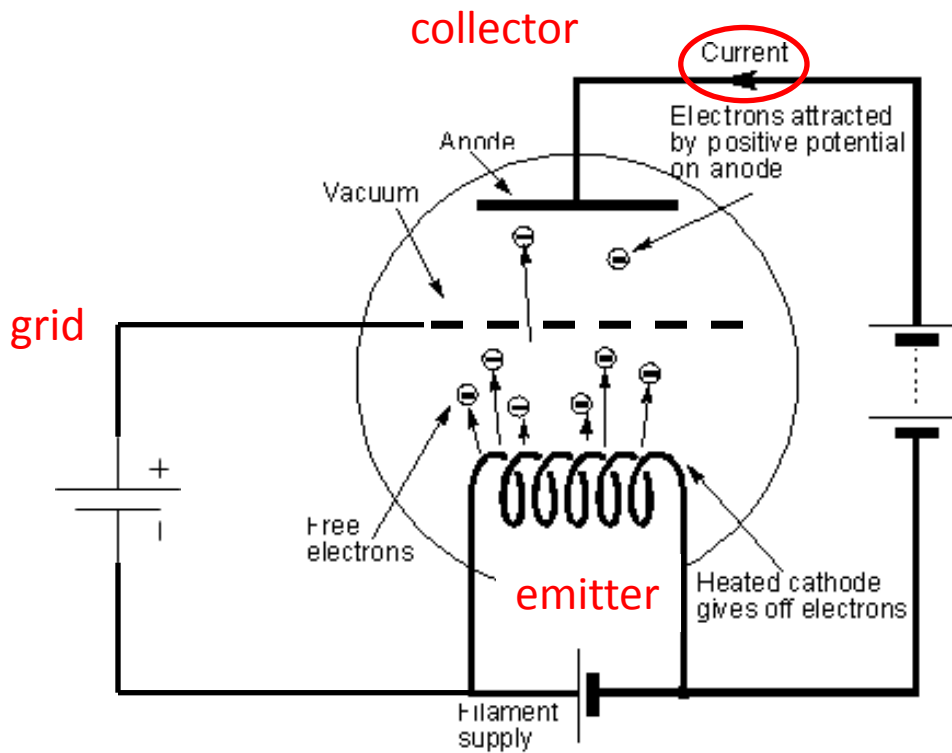

Transistors

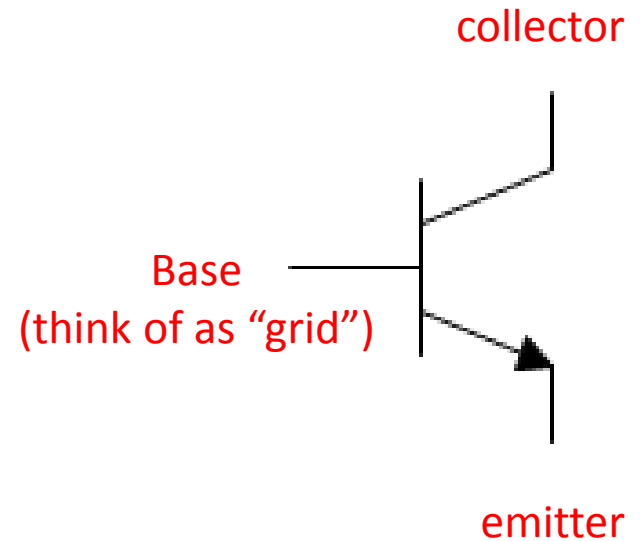

Small voltage on grid can block large current between emitter & collector.




Semiconductors


Transistors (bi-polar)

Transistors come in two flavors, “nnp” & “pnp”.

Symbol:

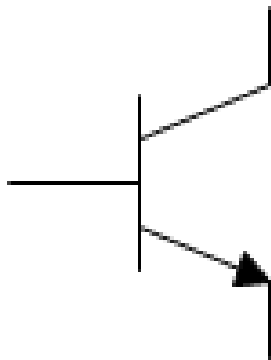

nnp

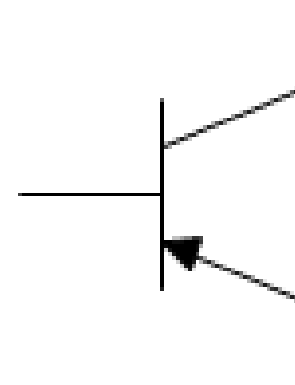



pnp

Handy mnemonic: “**N**ot **P**ointed **iN**”



Semiconductors

First Transistor

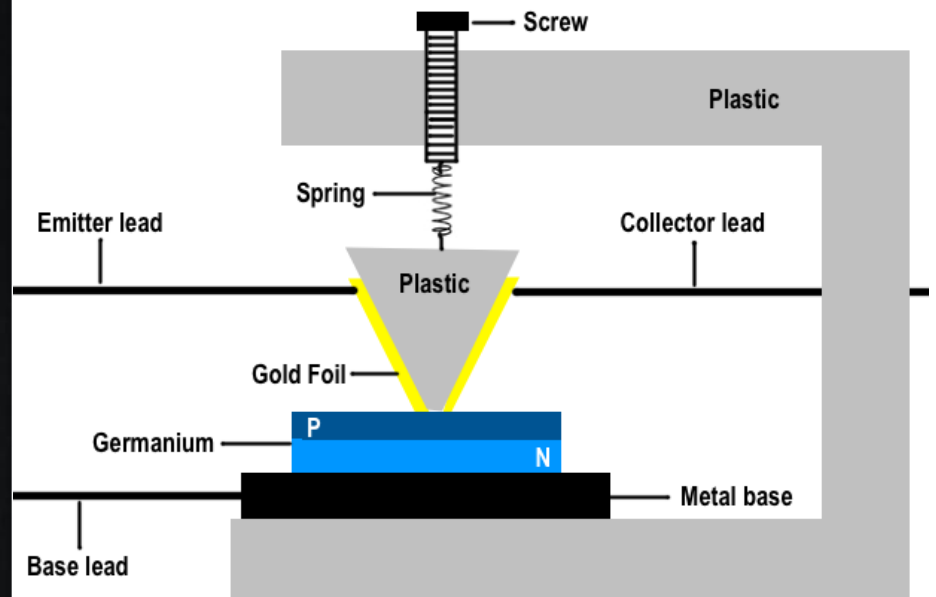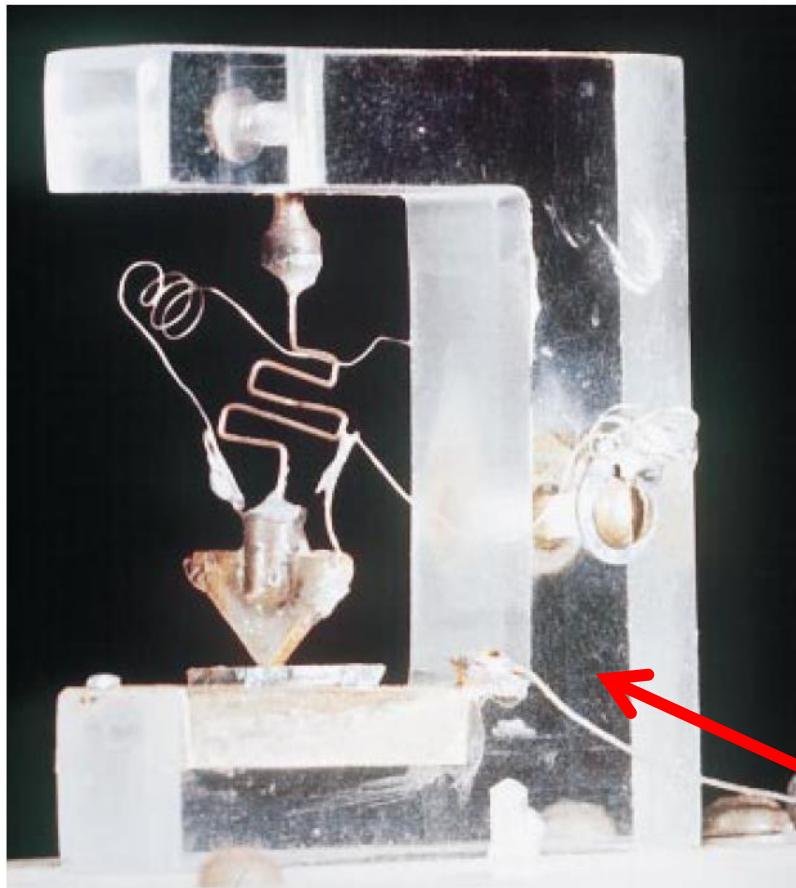


Yes, that is what a Physics Nobel Prize winning experiment looks like.



Semiconductors

Transistors (bi-polar)


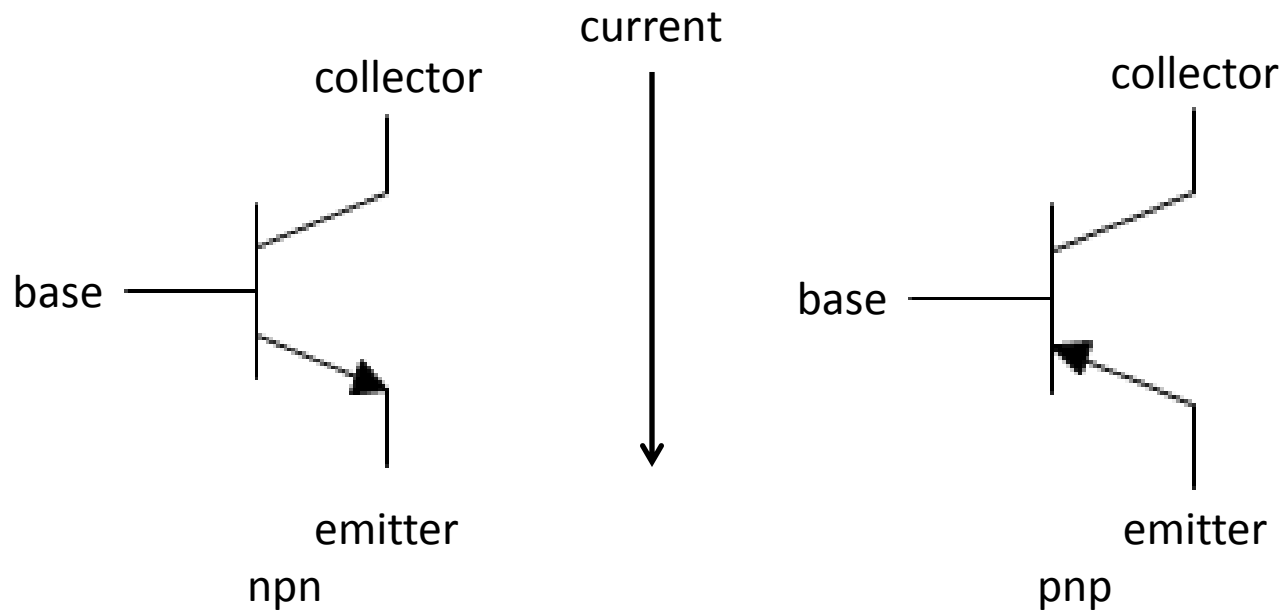


Convention is to always draw transistors with the current flowing down.



Semiconductors

Transistors (bi-polar)

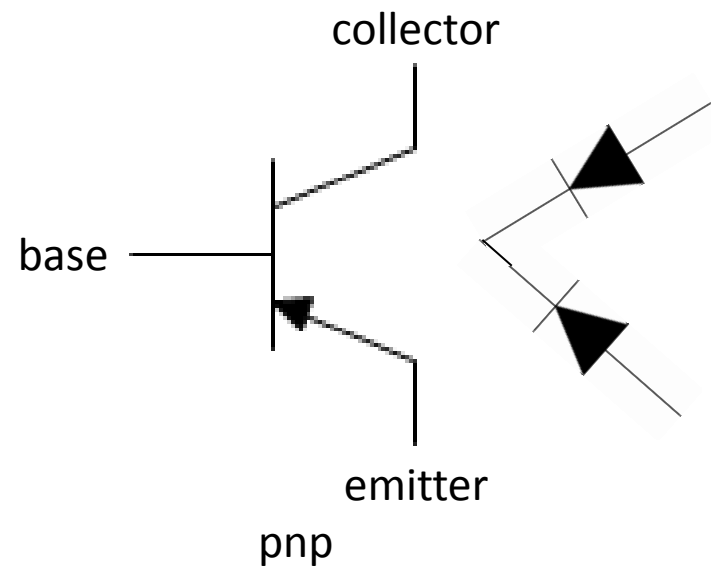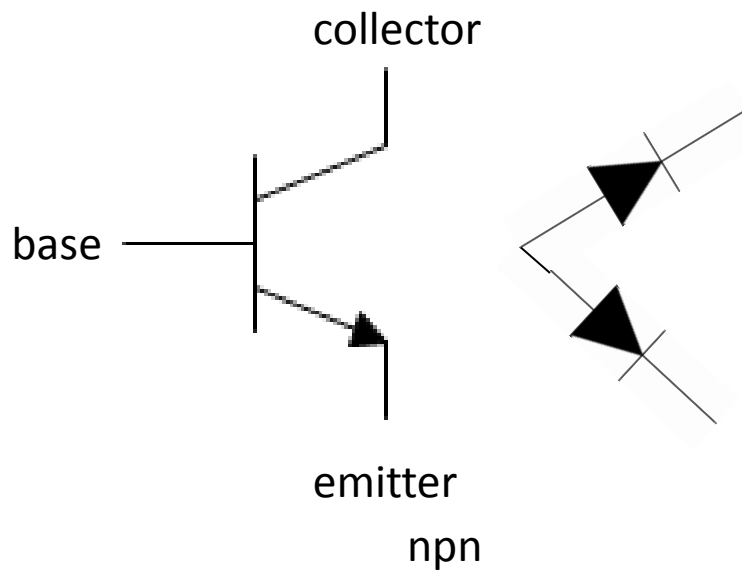


For certain intuitive purposes, one can think about these as weird diode pairs.




Semiconductors

Transistors (bi-polar)

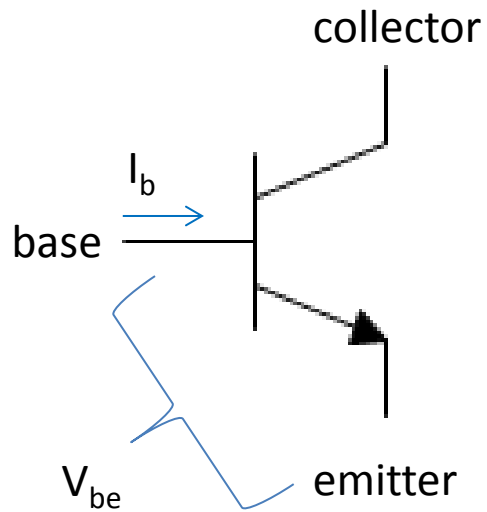

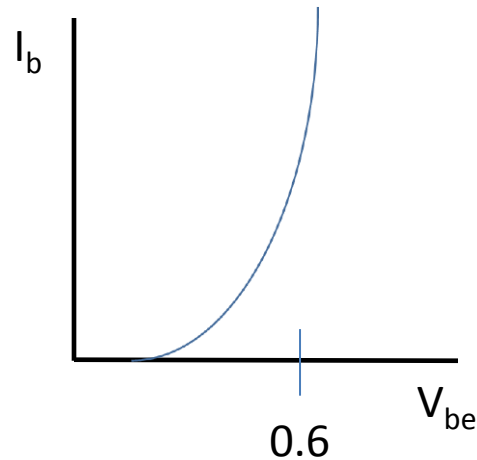
a) Base-emitter “diode” is forward biased. Therefore V_{be} clamped at $\sim 0.6V$ for a silicon transistor.





Semiconductors

Transistors (bi-polar)

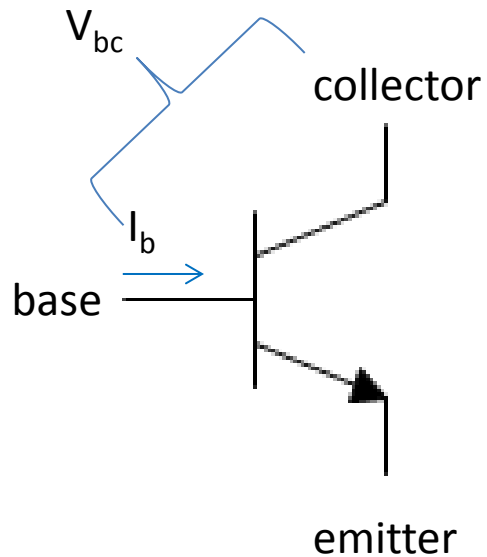

b) Base-collector “diode” is reverse biased.


Therefore $I_{bc} \cong 0$ (all base current flows through emitter).

Therefore V_{bc} can vary.



Semiconductors

Transistors (bi-polar)

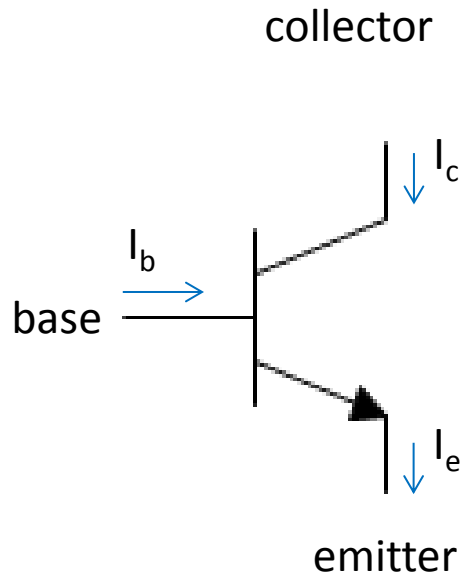

c) When I_b flows into a base-emitter circuit.

$$I_c = \beta I_b \text{ or } I_c = h_{FE} I_b \text{ (There's two symbols in use.)}$$

Where $\beta \gg 1$ current gain just like in a vacuum tube.


Typical $\beta \sim 100$

$$I_e = I_c + I_b = I_c + I_c / \beta \cong I_c + I_c / 100 \cong 1.01 I_c \cong I_c$$



Semiconductors

Transistors (bi-polar)

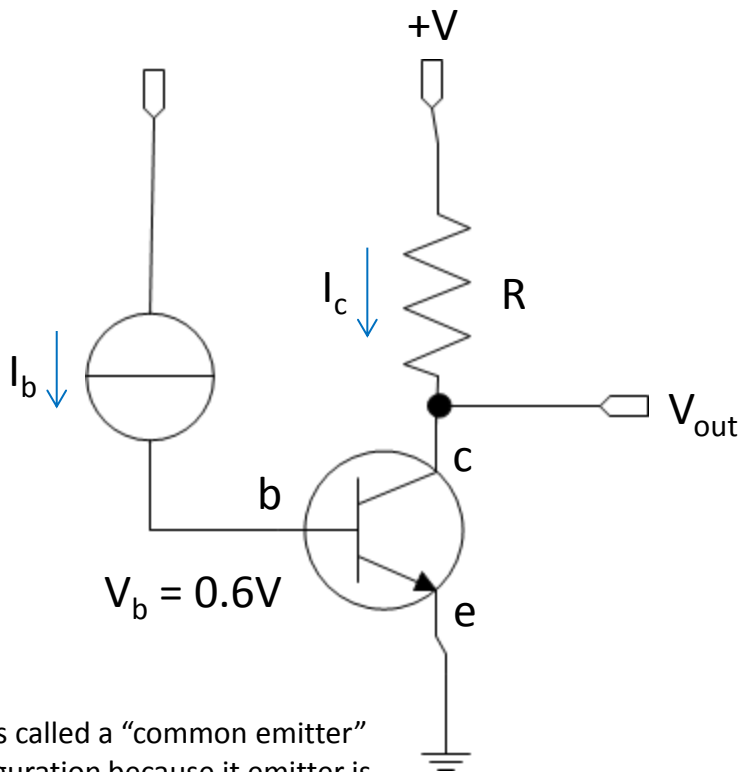

$$V_{out} = V - Ri_c$$

$$V_{out} > 0.6$$

Why? There is a forward biased “diode” between c & ground. (Through the b-e “forward biased diode”.)

$$I_c = \beta I_b$$

$$V_{out} = V - Ri_c$$


$$\therefore V_{out} = V - R\beta I_b$$

This is called a “common emitter” configuration because its emitter is “common” to both input & output voltages.



Semiconductors

Transistors (bi-polar)

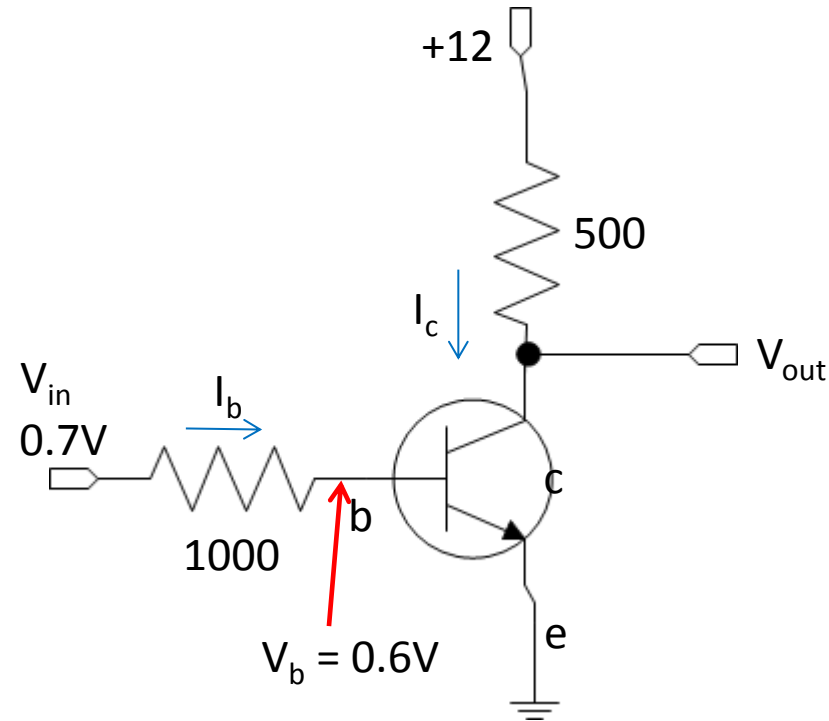

$$V_{out} = V - Ri_c$$

$$V_{out} > 0.6$$

Why? There is a forward biased “diode” between c & ground. (Through the b-e “forward biased diode”.)

$$I_c = \beta I_b$$

$$\therefore V_{out} = V - R\beta I_b$$

$$I_b = 0.1/1000 = 10^{-4}A, V = 12\text{volts}, R=500$$

Typical $\beta \sim 100$

$$V_{out} = 12 - 500 \cdot 10^2 \cdot 10^{-4} = 12 - 5 = 7 \text{ volts}$$



Semiconductors

Transistors (bi-polar)

More things to remember about transistors:

Current gain β typically ~ 100 , but can vary for the same transistor part number by factors of 2.

β Depends of temperature, current, voltage & frequency.

Transistors want certain voltage (biases) on the terminals. We use voltage dividers to do this.



Semiconductors

Transistors (bi-polar)

Nomenclature:



Absolute current & voltages are I & V (capital letters).

Signals are small changes in current & voltage are denoted as i & v , or di & dv that may sit on top of a steady voltage or current.



Semiconductors

Transistors (bi-polar)

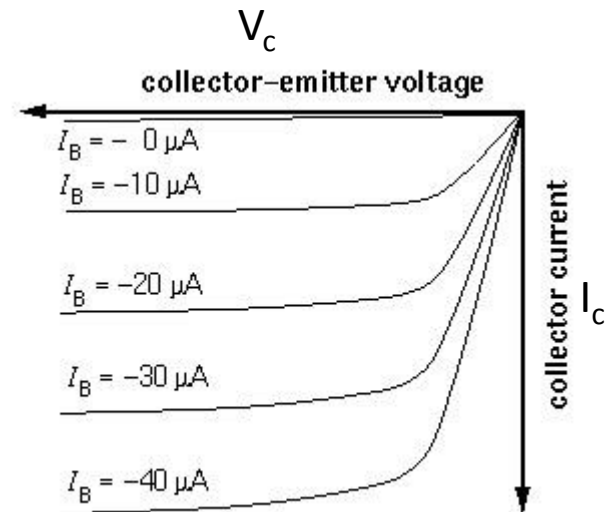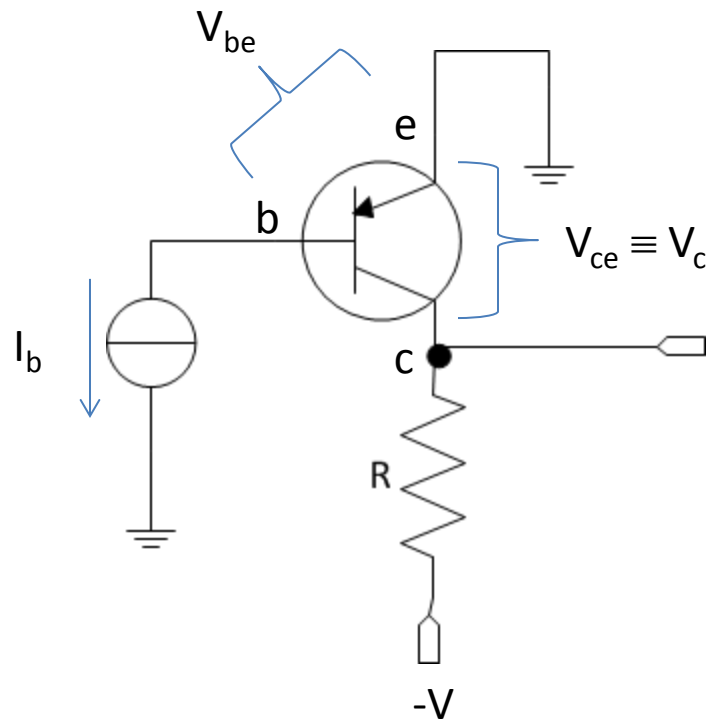

Looks like a diode curve translated along I_c in a controlled manner by I_b .




Semiconductors

Transistors (bi-polar)

Region where $I_b = 0$ (or negative) is called the cutoff region. The transistor resistance between c & e is very high.

Region where $I_c \cong \text{constant}$ & roughly linear in I_b is called the “active region”


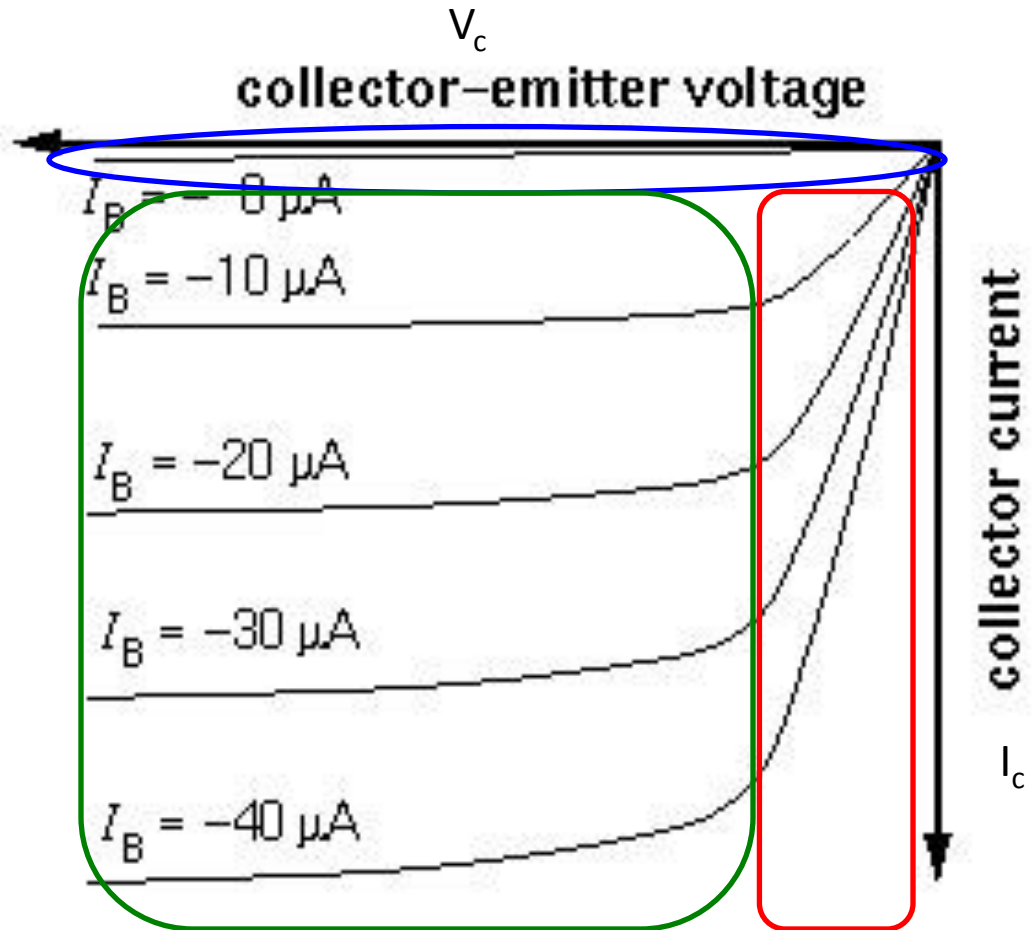
Region where the transistor is fully “on” is the saturation region & collector-emitter voltage looks “ohmic” (linear in current).





Semiconductors

Transistors (bi-polar)

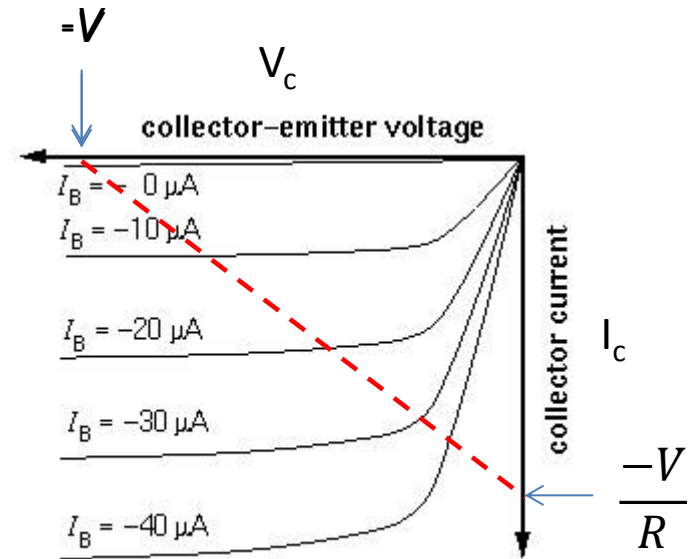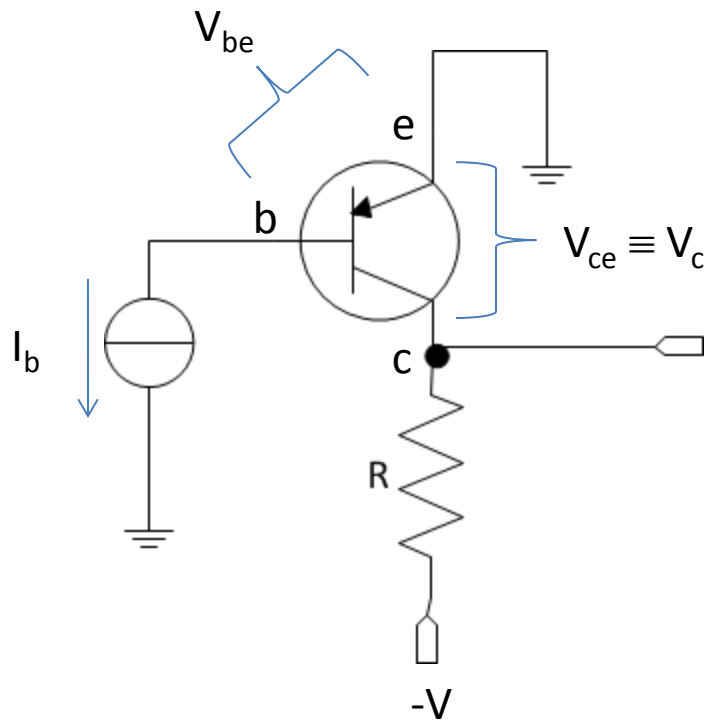

Dashed line is called a “load line”. As I_b is changed, I_c varies. V_c follows along this line.

$$V_{c \max} = -V \text{ (when } I_b=0\text{)}$$

$$I_{c \max} = -\frac{V}{R} \text{ (when transistor fully on)}$$




Semiconductors

Transistors (bi-polar) Common configurations

Common emitter (npn)

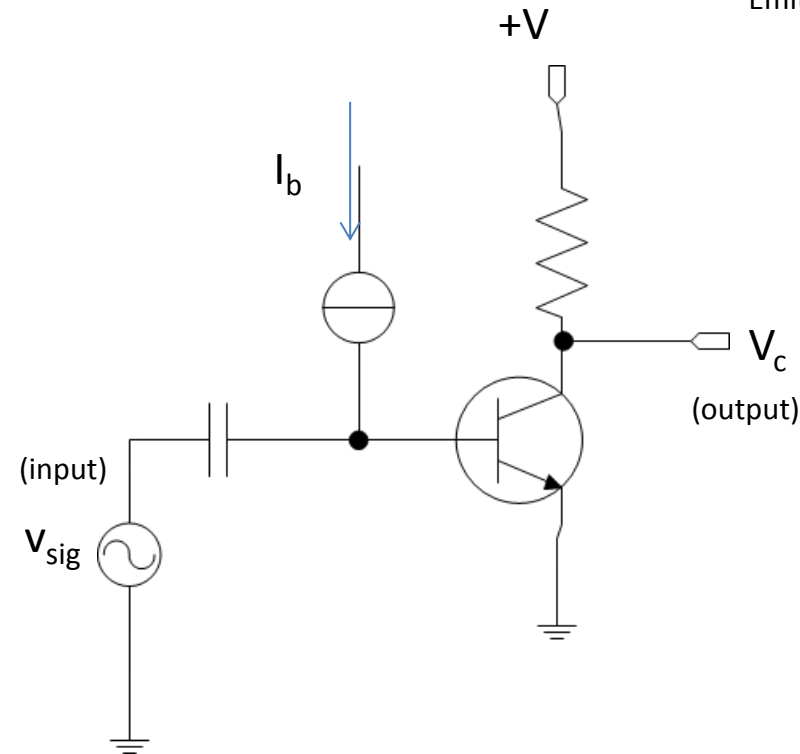Emitter is common (ground) for both the input signal & output signal



Voltage, current gain

Inverting (v_c 180° phase shift from v_{sig})

Midrange input & output impedances



Semiconductors

Transistors (bi-polar) Common configurations


Emitter follower

Current gain

Voltage gain ~ 1 (V_e always 1 diode drop from V_b)

Non-Inverting (v_e 0° phase shift from v_{sig})

Midrange input & output impedances

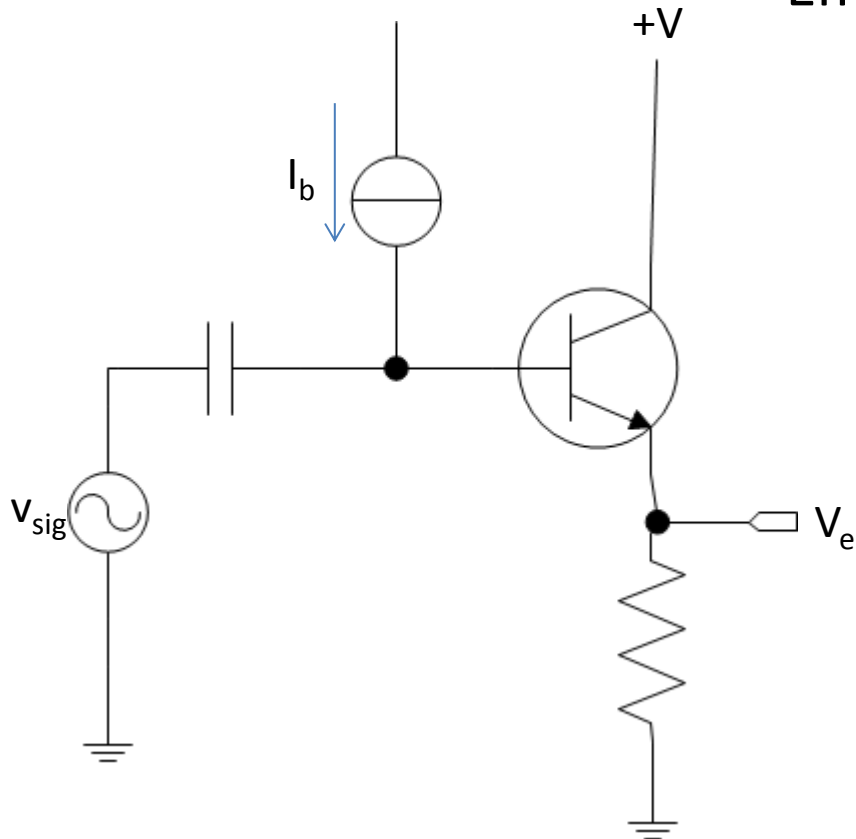




Semiconductors

Transistors (bi-polar) Common configurations

Common collector (pnp)

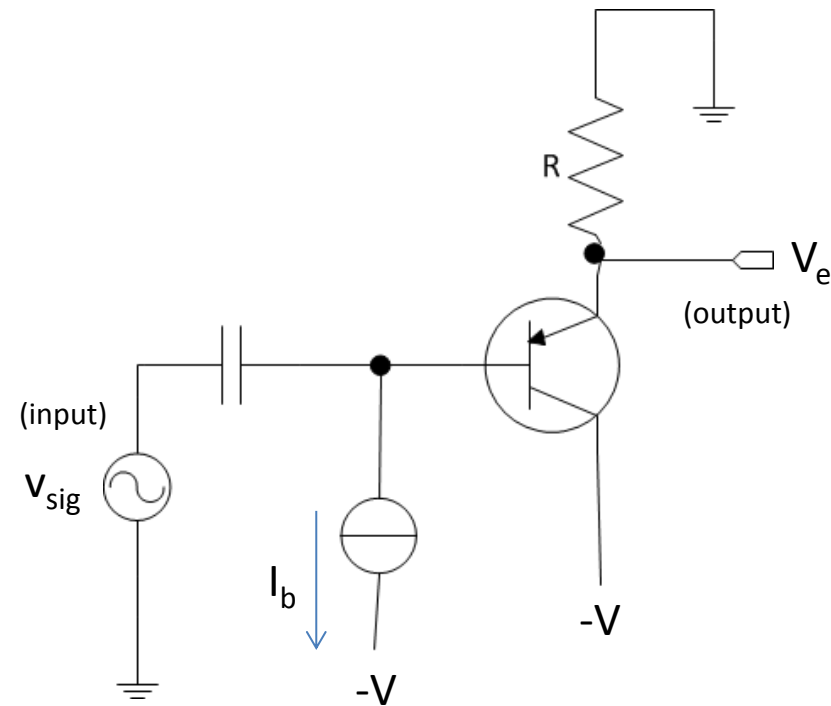Is the pnp transistor version of the emitter follower.



Current gain

Voltage gain ~ 1 (V_e always 1 diode drop from V_b)

Non-Inverting (v_e 0° phase shift from v_{sig})


Midrange input & output impedances



Semiconductors

Transistors (bi-polar) Common configurations

Common base (pnp)

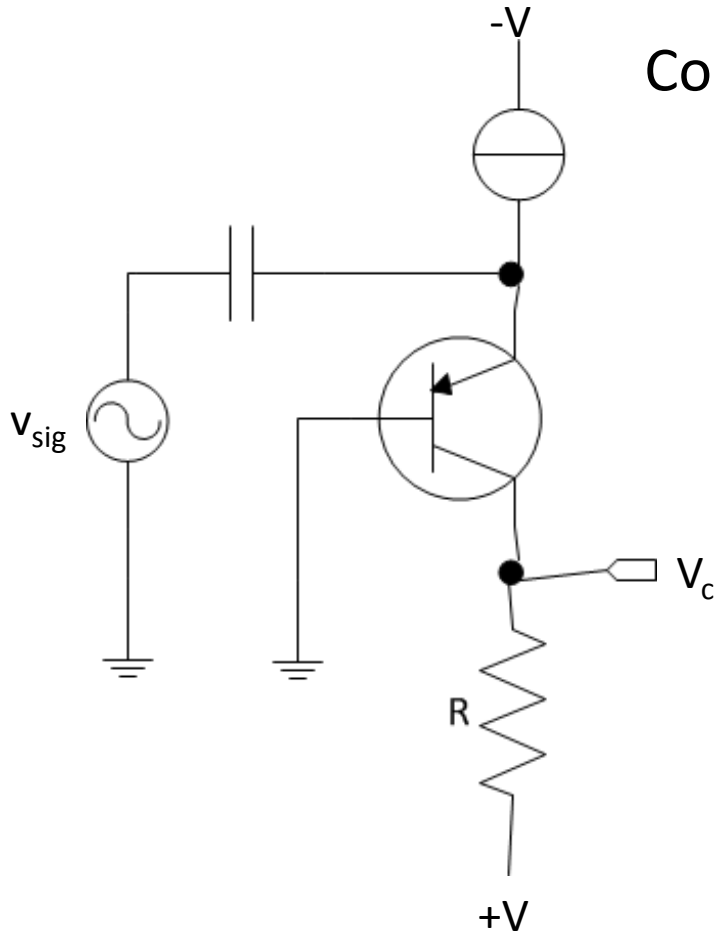

Voltage gain

Current gain ~ 1

Non-Inverting (v_c 0° phase shift from v_{sig})


Midrange input & output impedances



Semiconductors

Transistors (bi-polar) Real Example

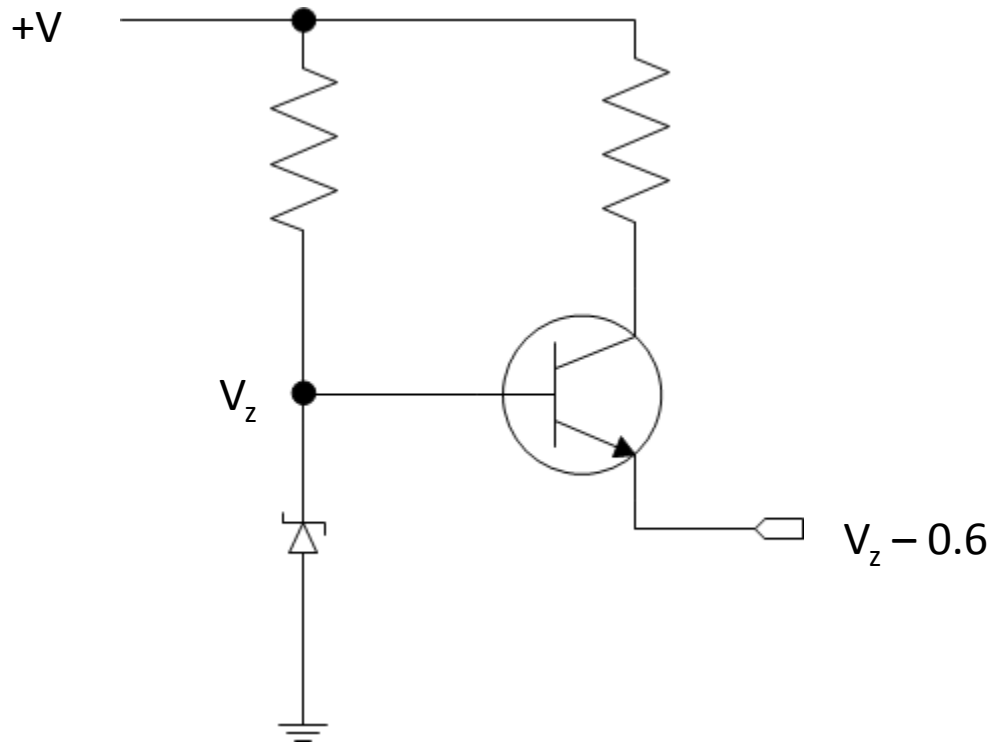Emitter follower voltage reference with higher current capability






Semiconductors

Diode Circuits

Regulated Full Wave Rectifier Power Supply

Example using real parts

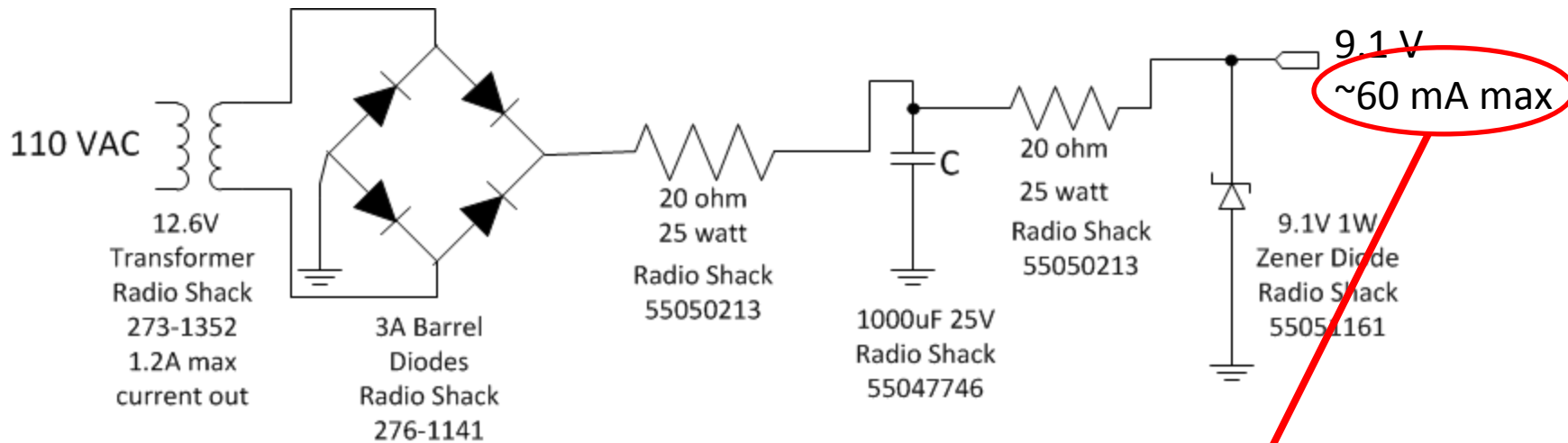

How do I know this?




Semiconductors

Diode Circuits

Regulated Full Wave Rectifier Power Supply

Example using real parts

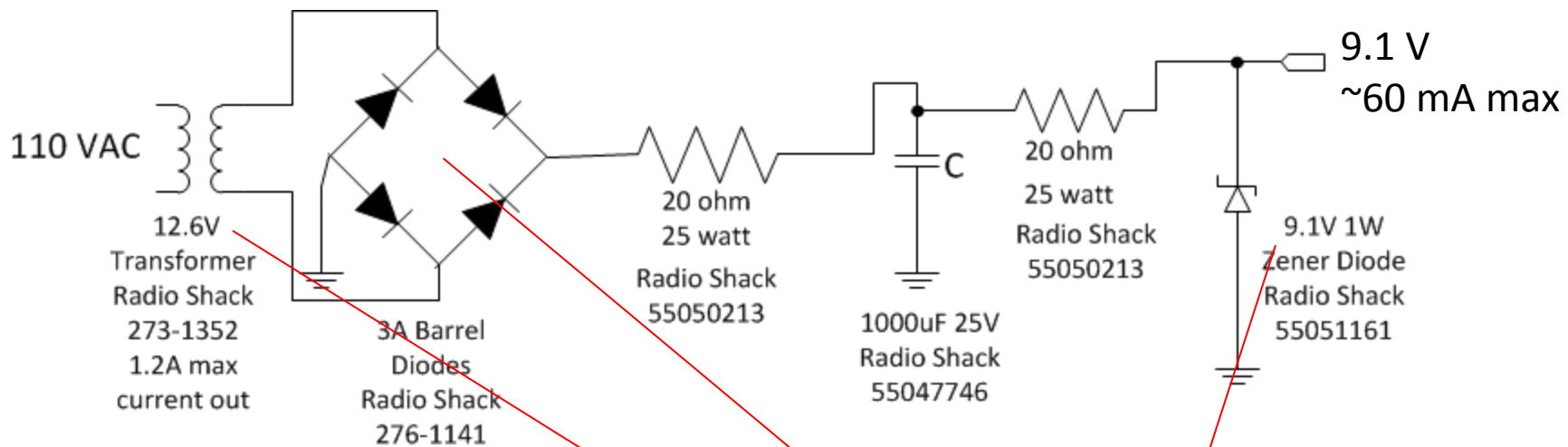

How do I know this?

$$12.6V - 1.2V - 9.1V = 2.3V$$




Semiconductors

Diode Circuits

Regulated Full Wave Rectifier Power Supply

Example using real parts

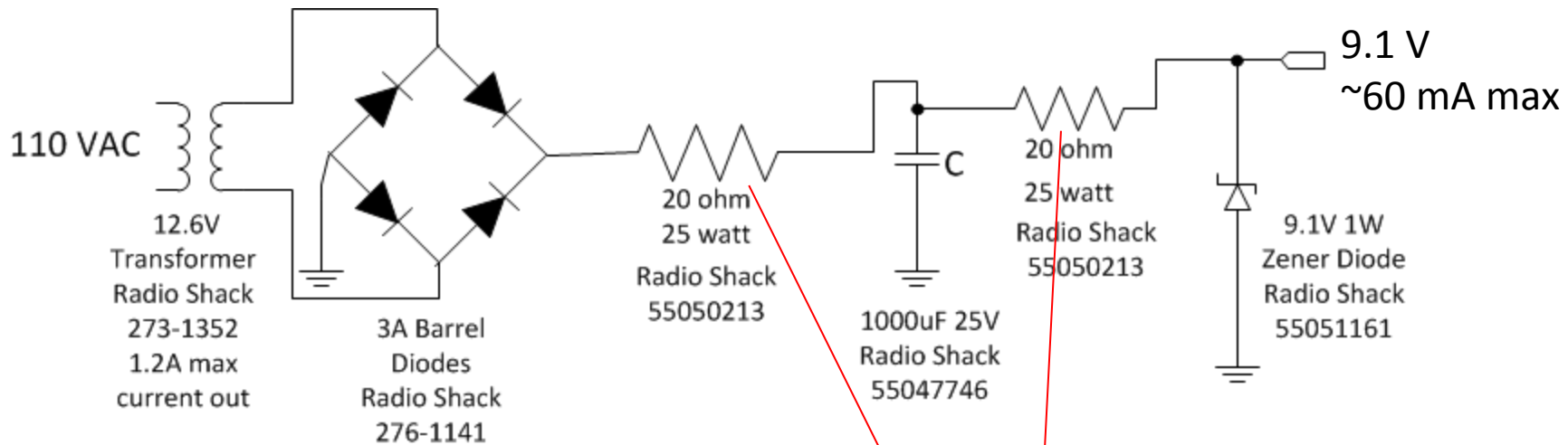

How do I know this?

$$12.6V - 1.2V - 9.1V = 2.3V$$


$$2.3V / 40 \text{ ohms} = 57.5\text{mA}$$



Semiconductors

Transistors (bi-polar) Real Example

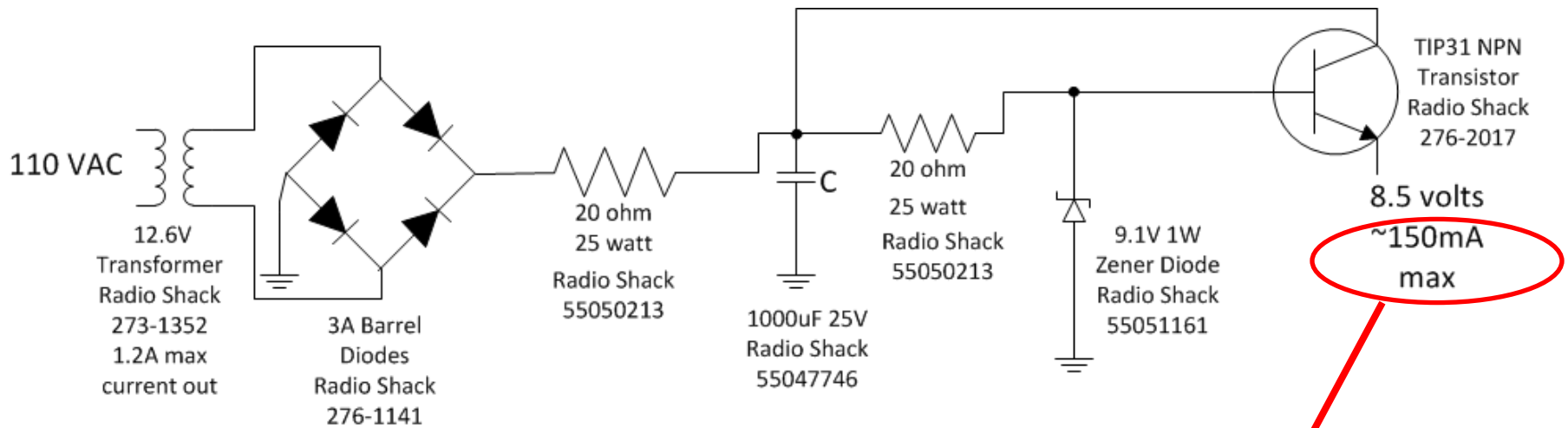Emitter follower voltage reference with higher current capability




How do I know this?



Semiconductors

Transistors (bi-polar) Real Example

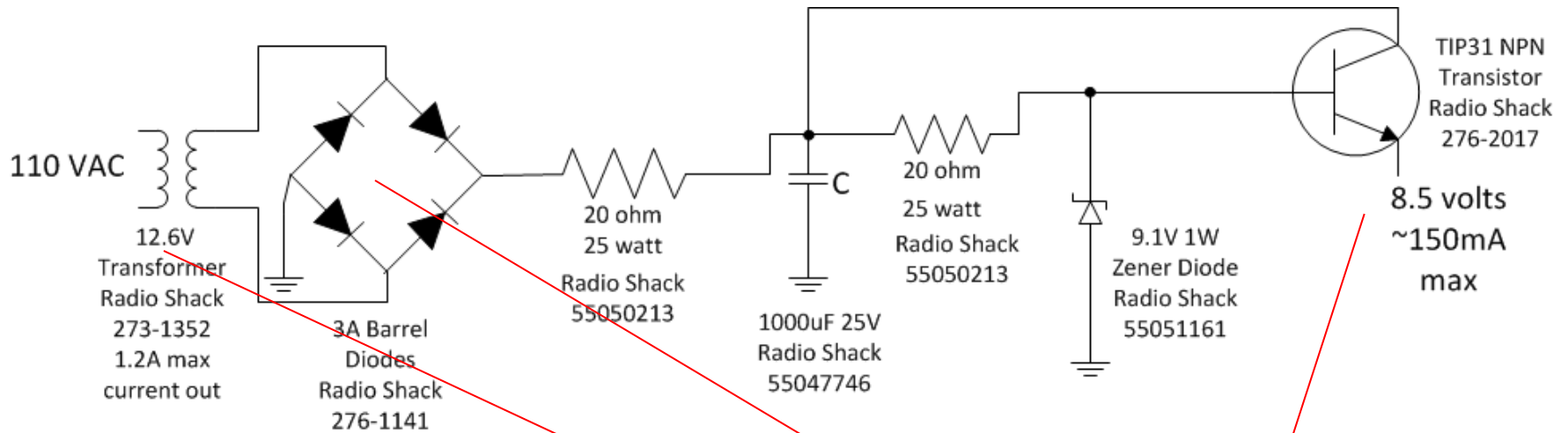Emitter follower voltage reference with higher current capability



How do I know this?


$$12.6V - 1.2V - 8.5V = 2.9V$$



Semiconductors

Transistors (bi-polar) Real Example

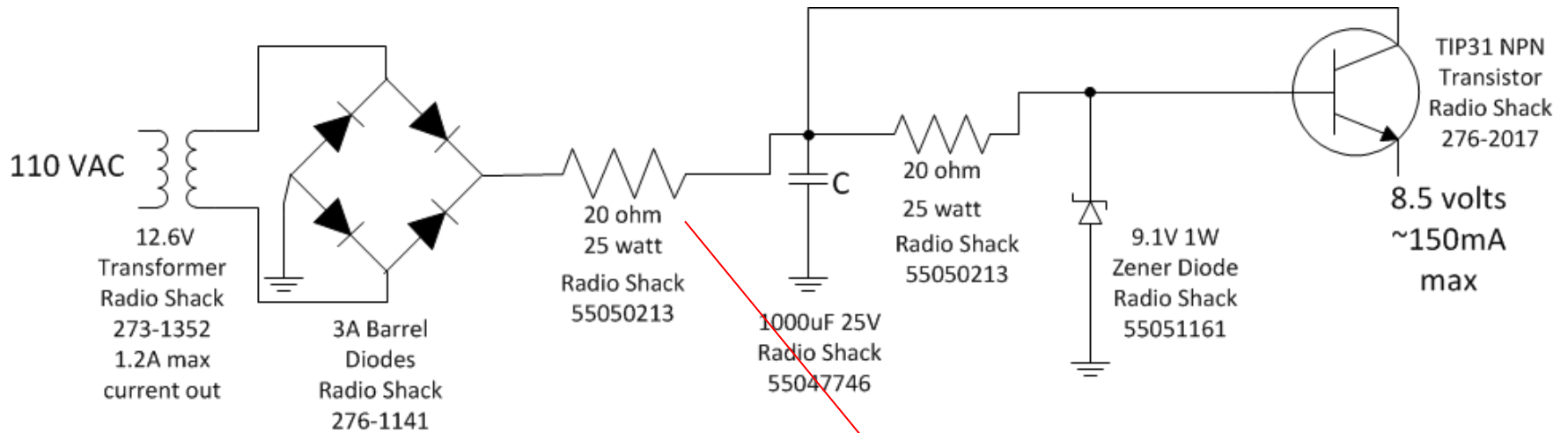Emitter follower voltage reference with higher current capability



How do I know this?

$$12.6V - 1.2V - 8.5V = 2.9V$$

$$2.9V / 20 \text{ ohms} = 145mA$$




Semiconductors

Transistors (bi-polar) Real Example

Common collector (npn)

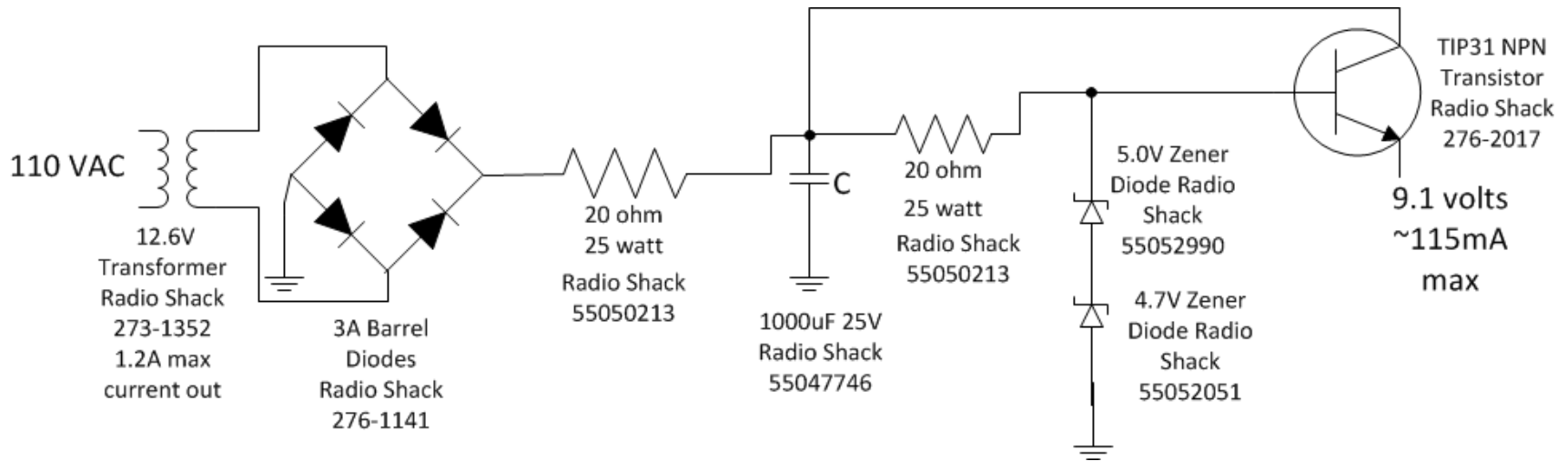Emitter follower voltage reference with higher current capability





Semiconductors

Transistors (bi-polar) Biasing

How/why bias the base?

We usually want to sit in the middle of the active region.



We want to control the transistor in a manner which will be insensitive to perturbations such as:

- **Variations in β with respect to temperature or part substitution.**
- **Variations in V_{be} . Although $V_{be} \sim 0.6V = 600mV$, it changes by $-2.5mV/^{\circ}K$.**



Semiconductors

Transistors (bi-polar) Bias

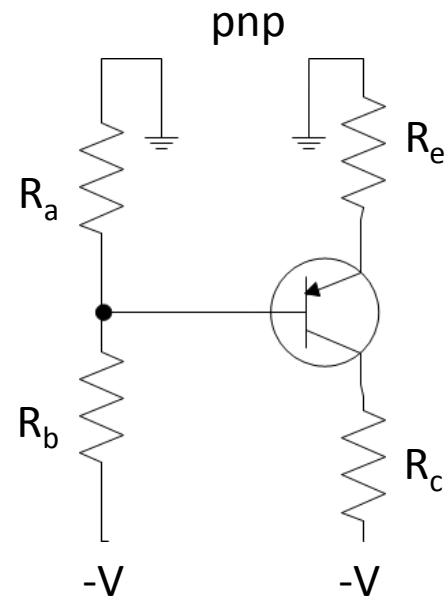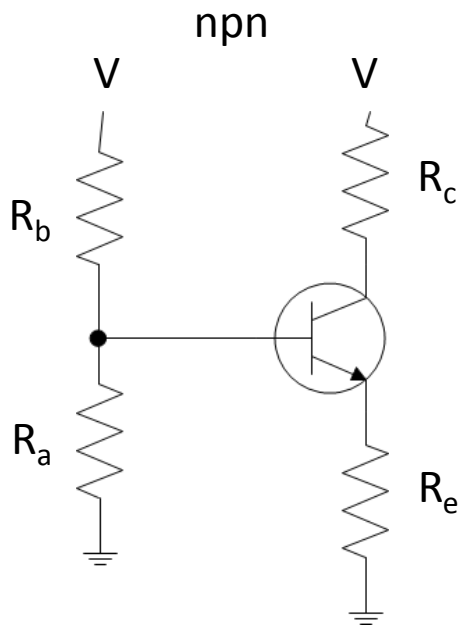


Bias the base-emitter junction by an external voltage divider.
We can choose R_a & R_b such that any signal is a small perturbation and we stay in the active region.



Semiconductors

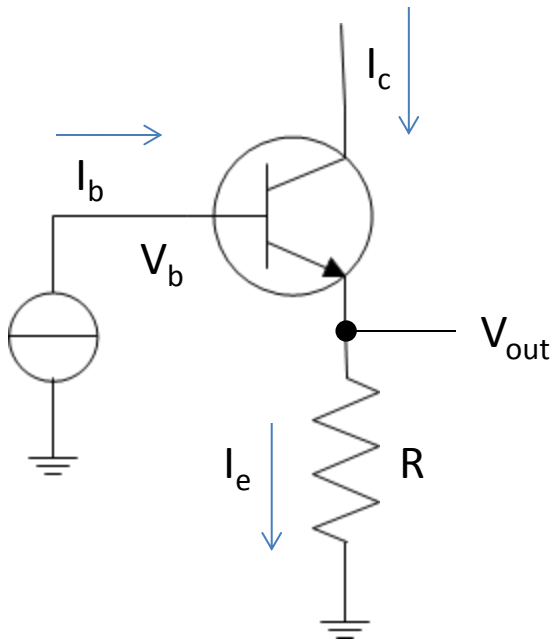Transistors (bi-polar) Input & Output Impedance



$$V_b = 0.6 + V_{out}$$

$$\Delta V_b = \Delta V_{out}$$

$$I_e = I_b + I_c, \quad I_c = \beta I_b \rightarrow I_e = I_b (1 + \beta)$$

$$\Delta I_e = (1 + \beta) \Delta I_b \text{ (current amplification)}$$

Input resistance:

$$r_{in} \equiv \frac{\Delta V_b}{\Delta I_b} = \frac{\Delta V_{out}}{\Delta I_b} = \frac{\Delta V_{out}}{\Delta I_e} (1 + \beta)$$

R

$$r_{in} = R (1 + \beta)$$

$$\beta \cong 100$$


More generally, $Z_{in} \cong (1 + \beta) Z_{load}$



Semiconductors

Transistors (bi-polar) Bias

How does this work?

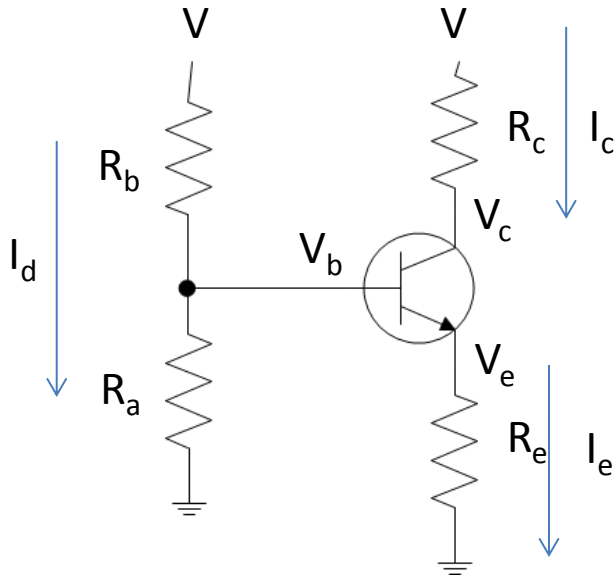

All voltages with respect to ground.

$$I_e = V_e / R_e$$

$$V_b = V_e + 0.6$$

$$V_c = V - I_c R_c$$

Suppose I_b is small compared to the divider current, $I_d \gg I_b$. (We can use small values for R_a & R_b .)

$$I_d = \frac{V}{R_a + R_b} \quad \text{We also know from our resistor voltage divider equation, that } V_b = V \frac{R_a}{R_a + R_b}.$$


$$\text{So } V_e = V \frac{R_a}{R_a + R_b} - 0.6 \quad \& \quad I_e = V_e / R_e = \frac{\left\{ V \frac{R_a}{R_a + R_b} - 0.6 \right\}}{R_e}. \quad \text{Also, } I_b \text{ is } I_c / \beta \quad \& \quad \beta \sim 100, \text{ so } I_c \cong I_e$$



Semiconductors

Transistors (bi-polar) How do we go about designing something?

Choose some things – calculate the rest

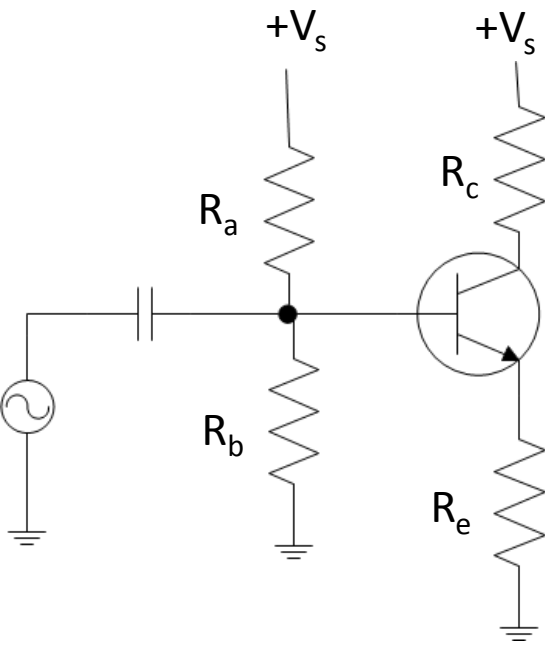

1) Choose Transistors

- Availability
- Current carrying capacity ($I_{C\text{MAX}}$)
- npn or pnp

2) Power Supply Voltage

- $V_s = V_{\text{supply}} < V_{ce\text{ MAX}}$ for chosen transistors

3) Operating Point (Bias circuit)

Want to operate in the active region.

$$I_c \leq \frac{1}{2} I_{C\text{MAX}}$$


$$V_c \approx \frac{1}{2} V_s$$

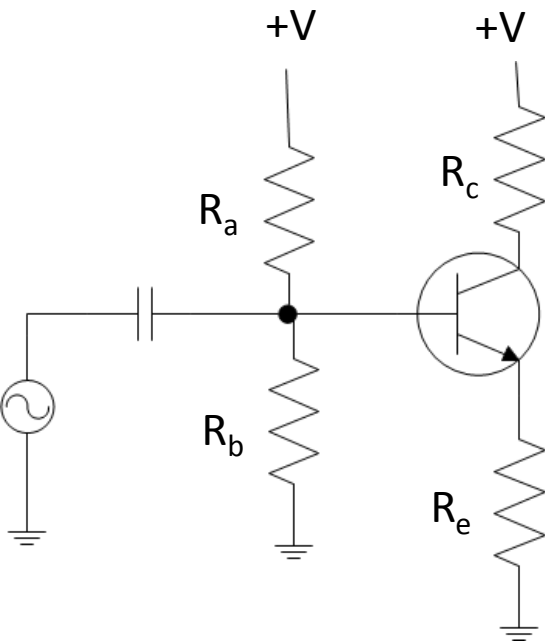4) V_e on the order of 1 volt, typically $\sim 1/20 V_s$



Semiconductors

Transistors (bi-polar) How do we go about designing something?



Suppose our Box 'O Transistors from Radio Shack says:


β Or $h_{FE} = 100 @ I_C = 10\text{ma}$

And we have a 30 volt power supply.



Semiconductors

Transistors (bi-polar) Quick & Dirty

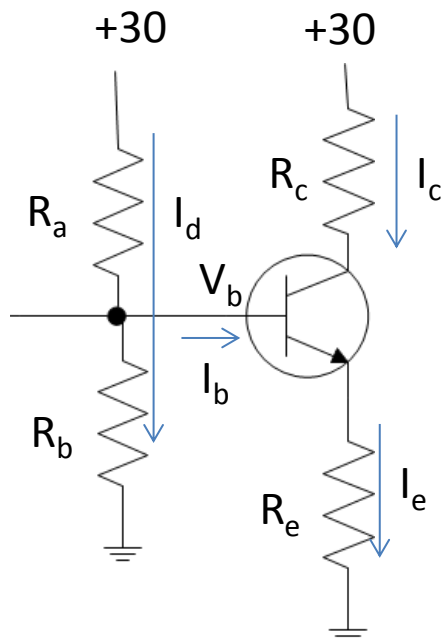

Choose $V_e = 1$ volt. So $V_b = V_e + 0.6 = 1.6$ volts

Want $I_d \gg I_b$, so the voltage divider isn't perturbed by I_b

I_b is on the order of μ amps, so lets set $I_d = 1\text{ma}$

$$(R_a + R_b)I_d = 30 \text{ volts} \rightarrow (R_a + R_b) = 30\text{k}\Omega$$

$$V_b = V_{\text{divider}} = V_s \frac{R_b}{R_a + R_b} \rightarrow \frac{R_b}{R_a + R_b} = \frac{1.6}{30}$$


So $R_a = 28.4\text{k}\Omega$, $R_b = 1.6\text{k}\Omega$



Semiconductors

Transistors (bi-polar) Quick & Dirty

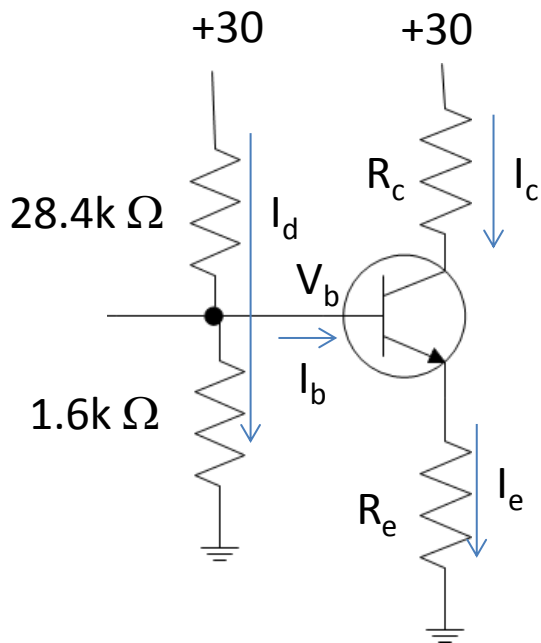So $R_a = 28.4k \Omega$, $R_b = 1.6k \Omega$



Set $V_c \approx \frac{1}{2} V_s = 15$ volts

We want to operate at $I_c = 10\text{ma}$ & we know $\beta \approx 100$,
So we know

$$R_e = \frac{V_e}{I_e} \cong \frac{V_e}{I_c} = \frac{1 \text{ volt}}{10 \text{ ma}} = 100\Omega$$

$$R_c = \frac{V_c}{I_c} = \frac{15 \text{ volts}}{10\text{ma}} = 1500 \Omega$$

Given typical resistor manufacturing tolerances, this is good enough.




Semiconductors

Transistors (bi-polar) Quick & Dirty

$$\text{So } R_a = 28.4\text{k } \Omega, R_b = 1.6\text{k } \Omega$$
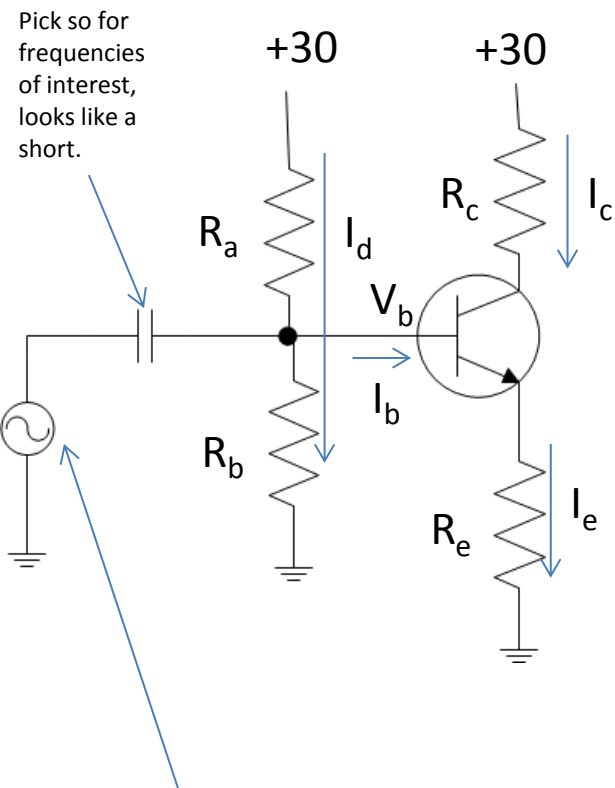
$$\text{Set } V_c \approx \frac{1}{2} V_s = 15 \text{ volts}$$



We want to operate at $I_c = 10\text{ma}$ so $\beta \approx 100$,
So we know

$$R_e = \frac{V_e}{I_e} \cong \frac{V_e}{I_c} = \frac{1 \text{ volt}}{100 \text{ ma}} = 100\Omega$$

$$R_c = \frac{V_c}{I_c} = \frac{15 \text{ volts}}{100 \text{ ma}} = 1500 \Omega$$

Input impedance for signal is $R_a || R_b || R_e (1 + \beta) \cong 1317 \Omega$.



Thursday, September 28 & Thursday, October 5

Lab 4 The Transistor Amplifier